

## Transformationseigenschaften eines idealen Transformators

| Bauelement         | Kettenform A  | Hybridform H  | Schaltung / Ersatzschaltung   |
|--------------------|---|---|-------------------------------|
| Z                  | $Z_1 = \frac{A_{11}}{A_{22}} \cdot Z_2$             | $Z_1 = H_{12} \cdot H_{21} \cdot Z_2$                       | <p>Kettenpfeilsystem</p>      |
| R                  | $R_1 = \frac{A_{11}}{A_{22}} \cdot R_2$             | $R_1 = H_{12} \cdot H_{21} \cdot R_2$                       |                               |
| L                  | $L_1 = \frac{A_{11}}{A_{22}} \cdot L_2$             | $L_1 = H_{12} \cdot H_{21} \cdot L_2$                       |                               |
| C                  | $C_1 = \frac{A_{22}}{A_{11}} \cdot C_2$             | $C_1 = \frac{1}{H_{12} \cdot H_{21}} \cdot C_2$             |                               |
| Reihen-Schaltung   | $Z_1 = \frac{A_{11}}{A_{22}} \cdot (Z_2^1 + Z_2^2)$ | $Z_1 = H_{12} \cdot H_{21} \cdot (Z_2^1 + Z_2^2)$           |                               |
| Parallel-Schaltung | $Y_1 = \frac{A_{22}}{A_{11}} \cdot (Y_2^1 + Y_2^2)$ | $Y_1 = \frac{1}{H_{12} \cdot H_{21}} \cdot (Y_2^1 + Y_2^2)$ |                               |
| f                  | $f_2 = \frac{1}{A_{22}} \cdot f_1$                  | $f_2 = H_{21} \cdot f_1$                                    |                               |
| e                  | $e_2 = \frac{1}{A_{11}} \cdot e_1$                  | $e_2 = \frac{1}{H_{12}} \cdot e_1$                          | <b>Umrechnung Tor1 / Tor2</b> |

## Transformationseigenschaften eines idealen Gytrators

| Baelement          | Kettenform A  | Admittanzform Y   | Schaltung / Ersatzschaltung   |
|--------------------|---|---|-------------------------------|
| Z                  | $Z_1 = \frac{A_{12}}{A_{21}} \cdot Y_2$             | $Z_1 = \frac{1}{Y_{12} \cdot Y_{21}} \cdot Y_2$             | <p>Kettenfeilsystem</p>       |
| R                  | $R_1 = \frac{A_{12}}{A_{21}} \cdot G_2$             | $R_1 = \frac{1}{Y_{12} \cdot Y_{21}} \cdot G_2$             |                               |
| L                  | $L_1 = \frac{A_{12}}{A_{21}} \cdot C_2$             | $L_1 = \frac{1}{Y_{12} \cdot Y_{21}} \cdot C_2$             |                               |
| C                  | $C_1 = \frac{A_{21}}{A_{12}} \cdot L_2$             | $C_1 = Y_{12} \cdot Y_{21} \cdot L_2$                       |                               |
| Reihen-Schaltung   | $Y_1 = \frac{A_{21}}{A_{12}} \cdot (Z_2^1 + Z_2^2)$ | $Z_1 = \frac{1}{Y_{12} \cdot Y_{21}} \cdot (Y_2^1 + Y_2^2)$ |                               |
| Parallel-Schaltung | $Z_1 = \frac{A_{12}}{A_{21}} \cdot (Y_2^1 + Y_2^2)$ | $Y_1 = Y_{12} \cdot Y_{21} \cdot (Z_2^1 + Z_2^2)$           |                               |
| f                  | $f_2 = \frac{1}{A_{12}} \cdot e_1$                  | $f_2 = Y_{21} \cdot e_1$                                    | <b>Umrechnung Tor1 / Tor2</b> |
| e                  | $e_2 = \frac{1}{A_{21}} \cdot f_1$                  | $e_2 = \frac{1}{Y_{12}} \cdot f_1$                          | <b>Umrechnung Tor1 / Tor2</b> |