

English Set as default language

- GENERAL / ELECTRONIC ORP / Redox / PH electrometer Shield for Wemos D1 Mini with LMP7721-ADS1115 ADM3260 29 SEP, 2019
- ELECTRONIC / UNSORTED Universal System Voltage Supervisor (SVS) - Voltage Monitors 18 SEP, 2019
- ELECTRONIC / UNSORTED LM5069 - Hot Swap Controller / Load Switch / Battery Switch 7 MAY, 2019
- ELECTRONIC / UNSORTED LTC3784 - 1200W Polyphase Boost Converter 13 MAR, 2019
- ELECTRONIC / UNSORTED 4.2" EPD E-Ink Display + ESP8266 - Wetter + Google Calendar 20 JUL, 2018

- CATEGORIES
- General
 - Class-D
 - Electronic
 - Finds
 - Media
 - Software
 - Unsorted

- DOWNLOADS
- Powerbank Comparison 20170709 (Downloads: 1.531)
 - BQ24450 Charger - Rev. 0.A (Downloads: 1.444)
 - Sanyanke SYK SMD Capacitors (Downloads: 1527)
 - Chang Huawei VT SMD Capacitors - Datasheet (Downloads: 1.486)
 - JWCO LM TH Capacitors - Datasheet (Downloads: 1.591)

ARCHIVES Select month

DATA PROTECTION Disable Google Analytics DSGVO (GDPR) Request personal data

10/30/50/100W LED application driver (UC3843A)


BY 360CUSTOMS · PUBLISHED 19 MAY 2014 · UPDATED 21 JANUARY 2016

The operation of power LEDs calls for constant current source for higher performance. (> 1A) As an example, of operating a 30W was shown LED to a modified Step-Up Converter (boost) here.

[Table of Contents](#)

One is to use 30W power led with the following parameters:

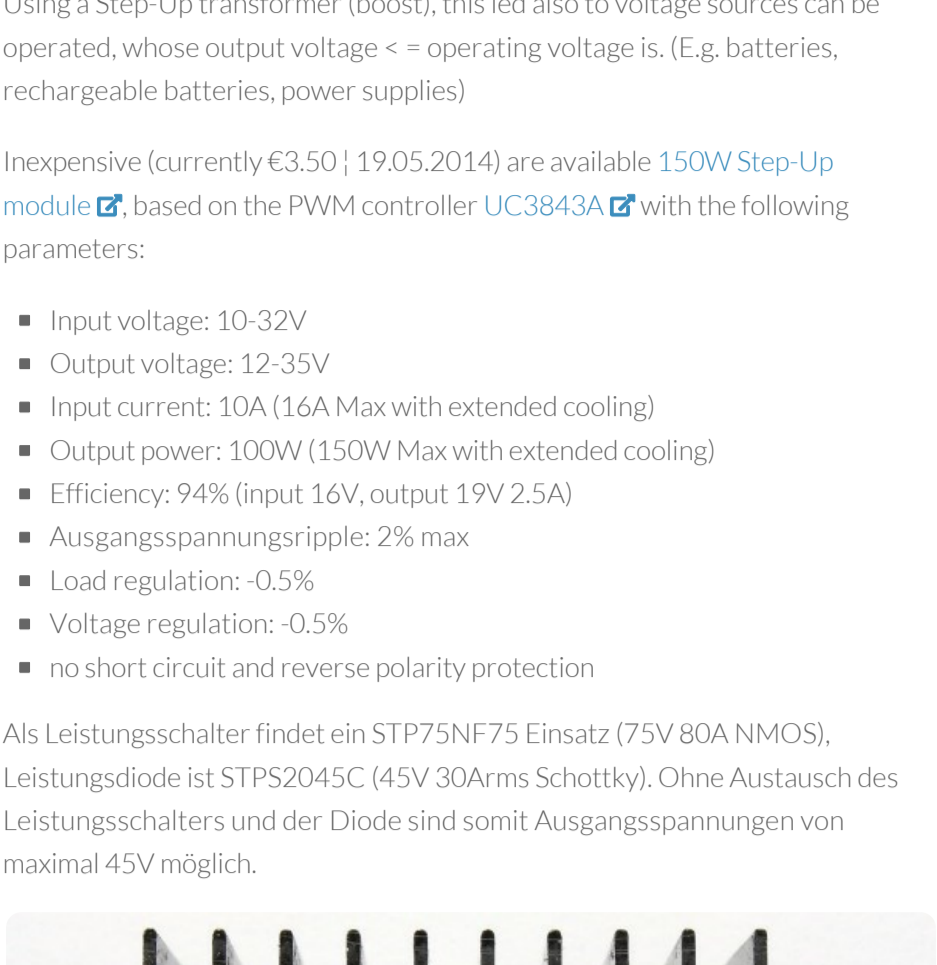- Power: 30W
- Color temperature: 3000-3500 k
- Operating voltage: 30-38V
- Operating current: 1A
- Light output: 2600-2800 lumens
- Life duration: > 50,000 hours




On the laboratory power supply, the operating current of 1A at approx. 38V adjusts itself. No constant current source is available, it can be operated LED with under voltage at low light output degradation. This voltage is selected, where the current is 10% less operating current (900mA). It is to make sure that the power, caused by thermal drift, specified does not exceed the operating current of the manufacturer.

Using a Step-Up transformer (boost), this led also to voltage sources can be operated, whose output voltage <= operating voltage is. (E.g. batteries, rechargeable batteries, power supplies)


Inexpensive (currently €3.50 | 19.05.2014) are available 150W Step-Up module, based on the PWM-controller UC3843A with the following parameters:

- Input voltage: 10-32V
- Output voltage: 12-35V
- Input current: 10A (1.6A Max with extended cooling)
- Output power: 100W (150W Max with extended cooling)
- Efficiency: 94% (input 16V, output 19V 2.5A)
- Ausgangsspannungsripple: 2% max
- Load regulation: -0.5%
- Voltage regulation: -0.5%
- no short circuit and reverse polarity protection

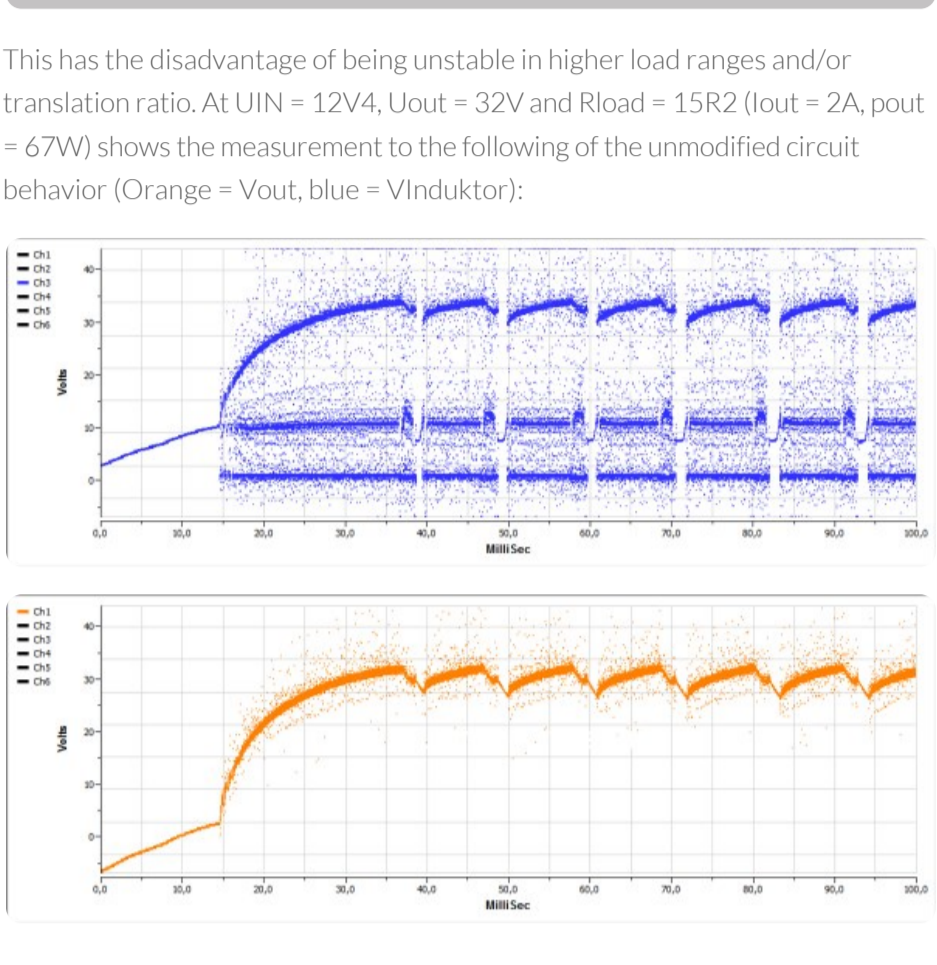
Als Leistungsschalter findet ein STP75NF75 Einsatz (75V 80A NMOS), Leistungsdiode ist STPS2045C (45V 30Arms Schottky). Ohne Austausch des Leistungsschalters und der Diode sind somit Ausgangsspannungen von maximal 45V möglich.



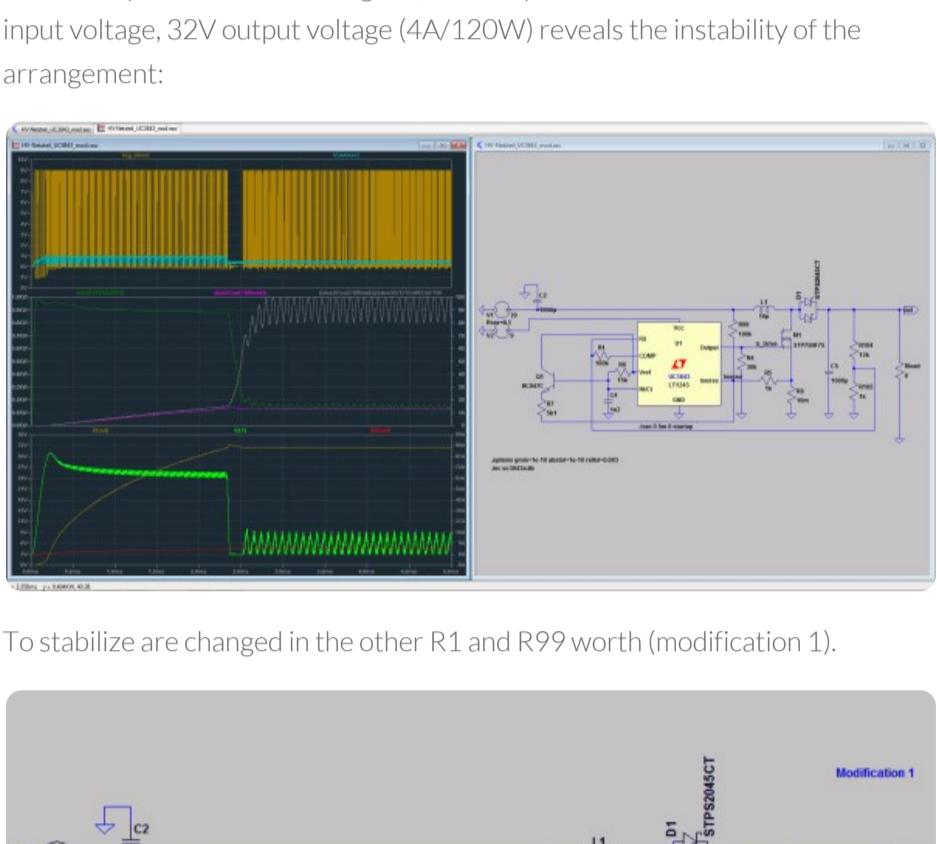Following figure shows the original circuit:




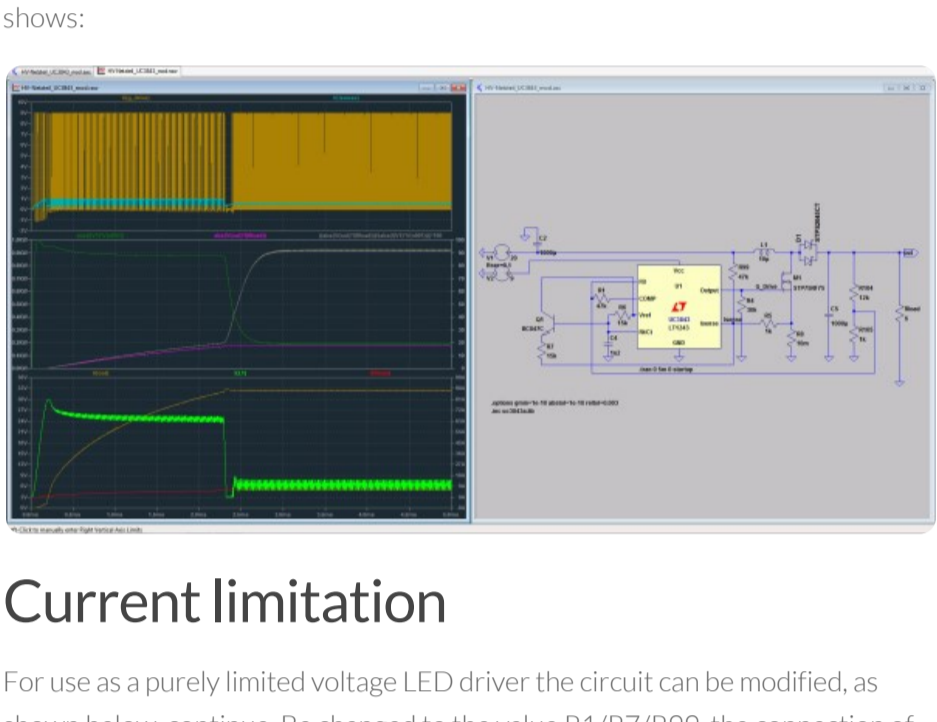This has the disadvantage of being unstable in higher load ranges and/or transition ratio. At UIN = 12V4, Uout = 32V and Rload = 15R2 (Iout = 2A, pout = 67W) shows the measurement to the following of the unmodified circuit behavior (Orange = Vout, blue = VInduktor):




Modification

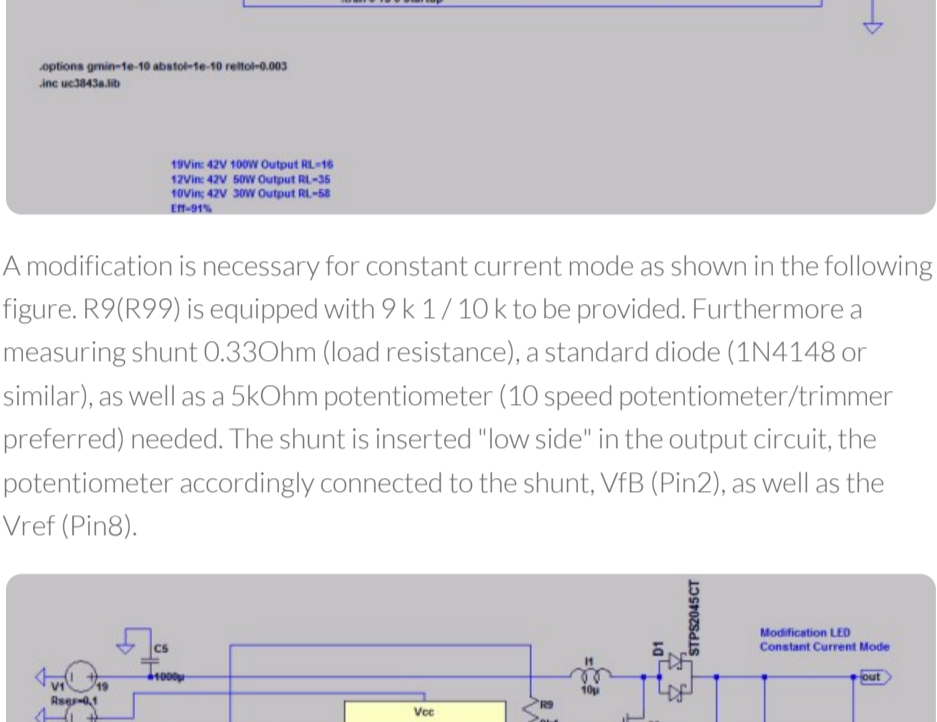
For subsequent simulation (original), C1 is replaced with a resistor (100k). 20V input voltage, 32V output voltage (4A/120W) reveals the instability of the arrangement:



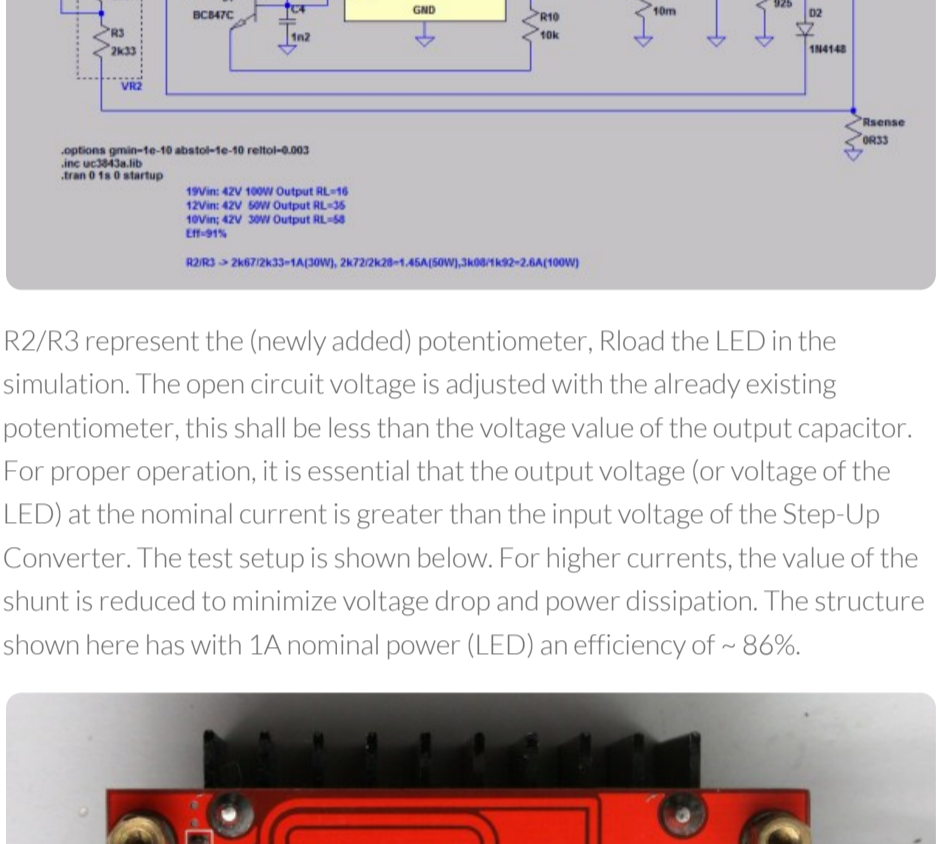To stabilize are changed in the other R1 and R99 worth (modification 1).




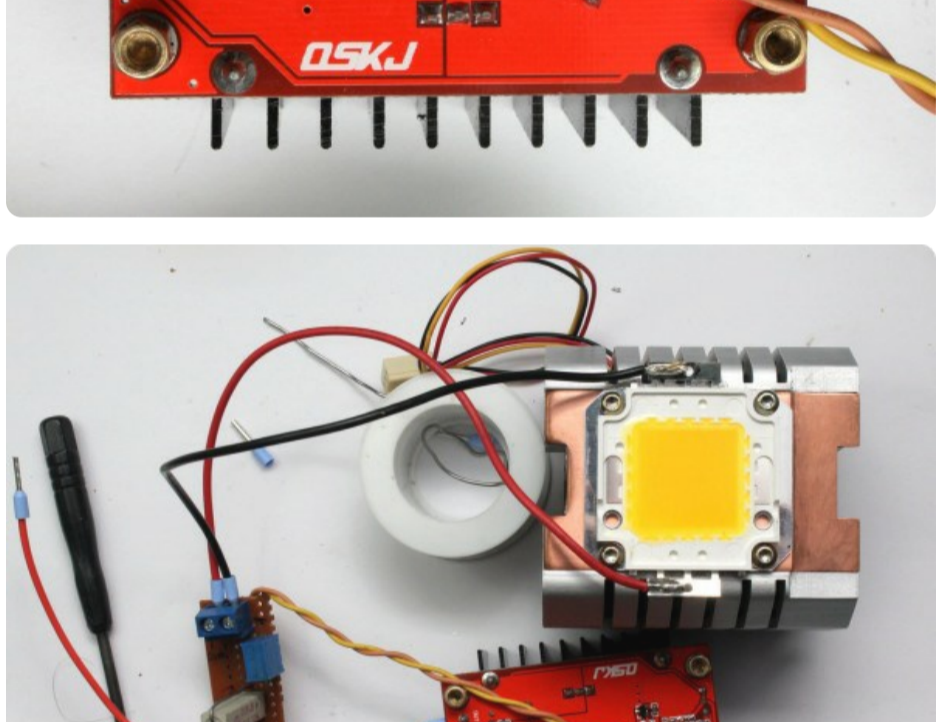The example simulation to 20V input voltage, output voltage (5A/160W) 32V shows:




Current limitation


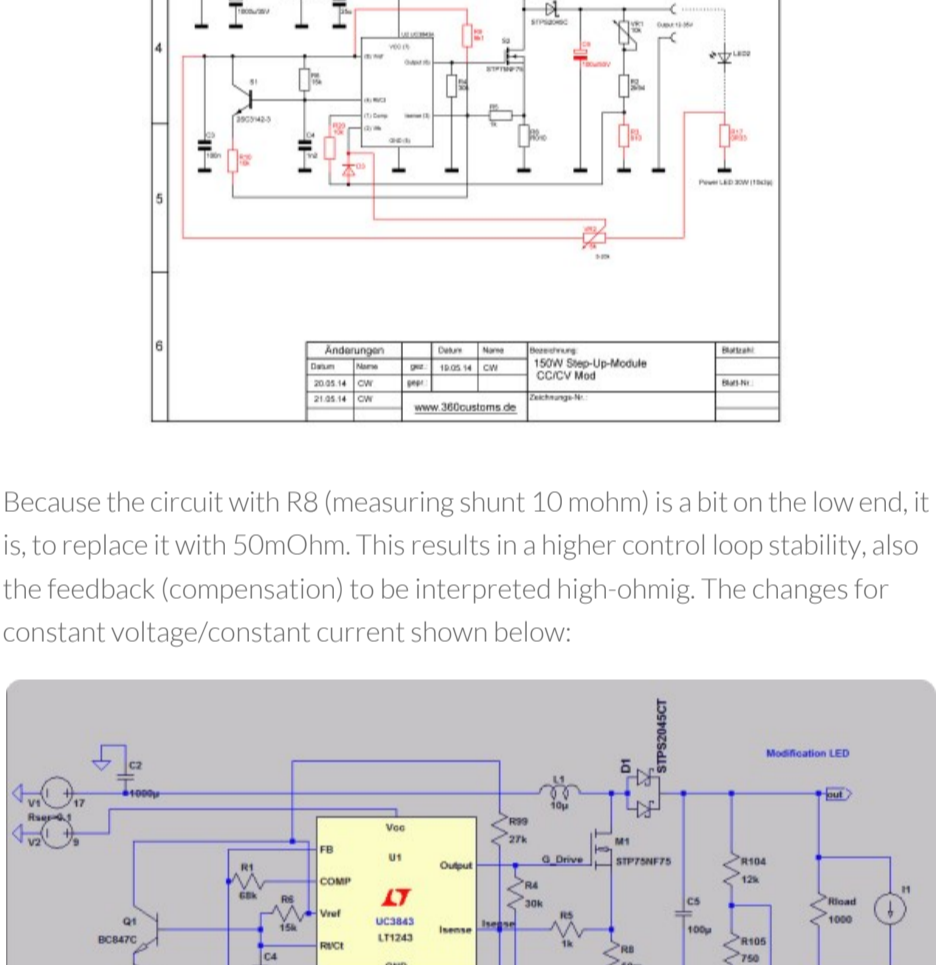
For use as a purely limited voltage LED driver the circuit can be modified, as shown below, continue. Be changed to the value R1/R7/R99, the connection of R99 is now on the 9V (7809). Note the minimum input voltage for different outputs.




A modification is necessary for constant current mode as shown in the following. R9(R99) is equipped with 9k 1 / 10k to be provided. Further more a measuring shunt 0.330hm (load resistance), a standard diode (1N4148 or similar), as well as a 5kOhm potentiometer (10 standard potentiometer/trimmer preferred) needed. The shunt is inserted "low side" in the output circuit, the potentiometer accordingly connected to the shunt, VFB (Pin2), as well as the Vref (Pin8).

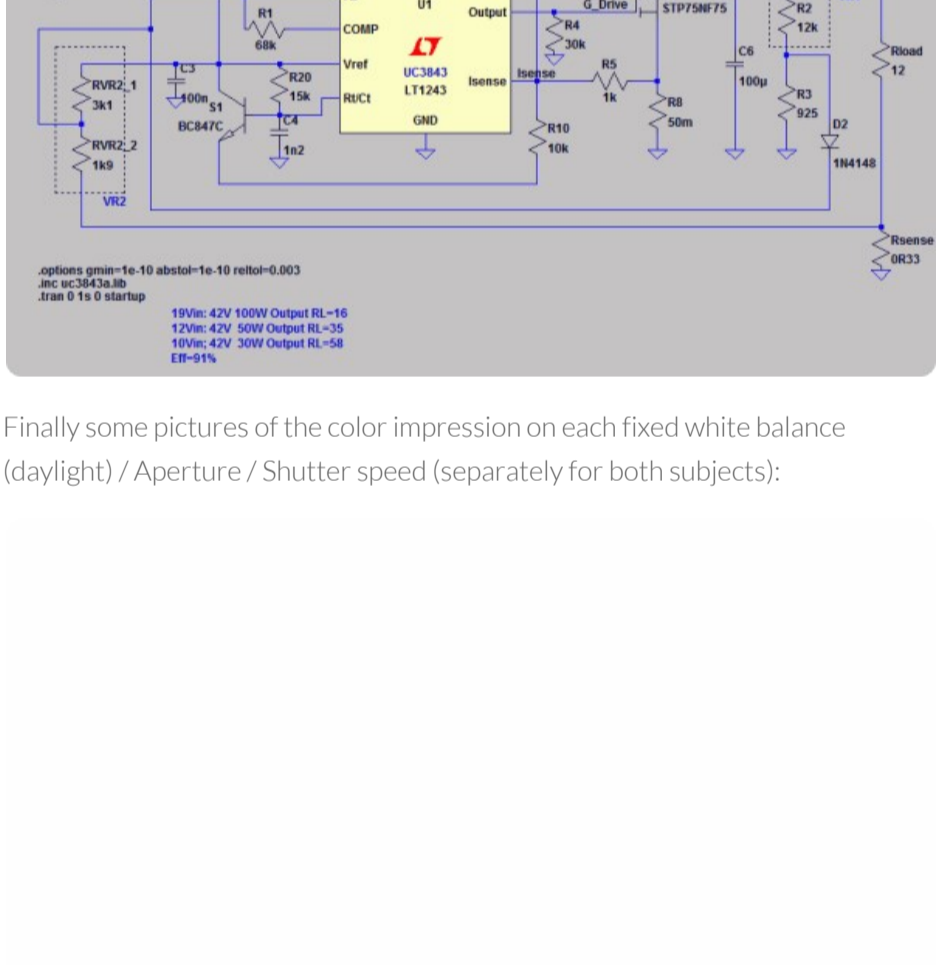



R2/R3 represent the (newly added) potentiometer, Rload the LED in the simulation. The open circuit voltage is adjusted with the already existing potentiometer, this shall be less than the voltage value of the output capacitor. For proper operation, it is essential that the output voltage (or voltage of the LED) at the nominal current is higher than the input voltage of the Step-Up Converter. The test setup is shown below. For higher currents, the value of the shunt is reduced to minimize voltage drop and power dissipation. The structure shown here has with 1A nominal power (LED) an efficiency of ~ 86%.

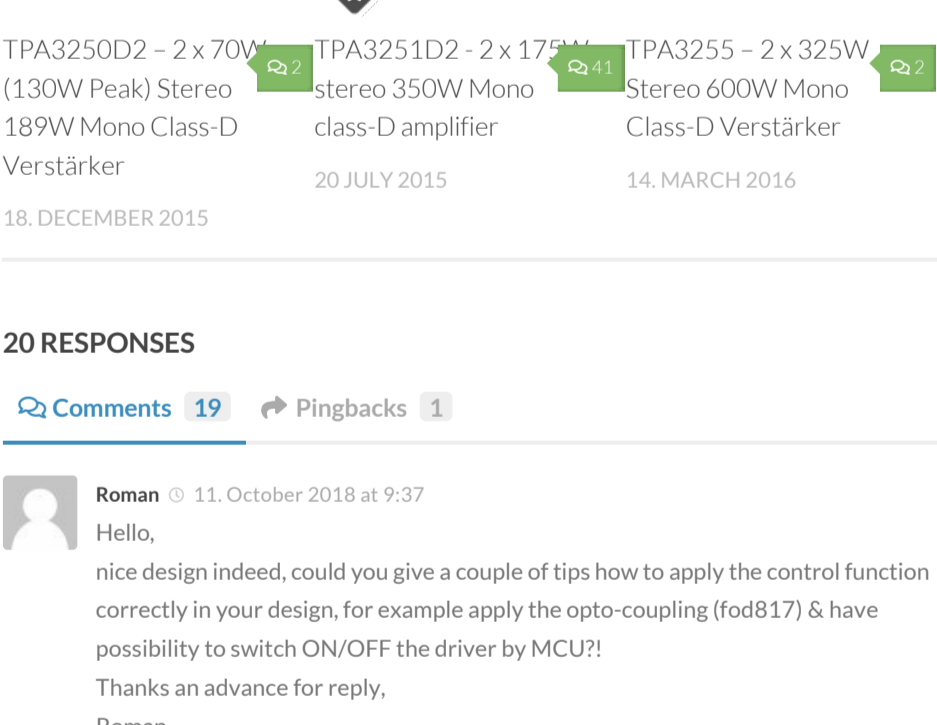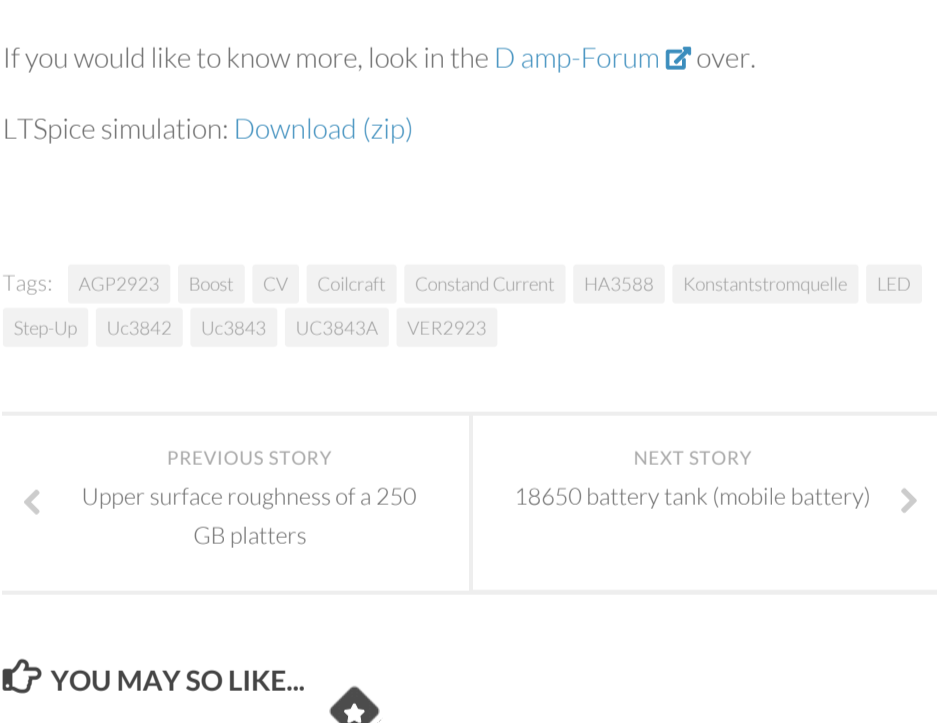


The circuit tag in the summary:

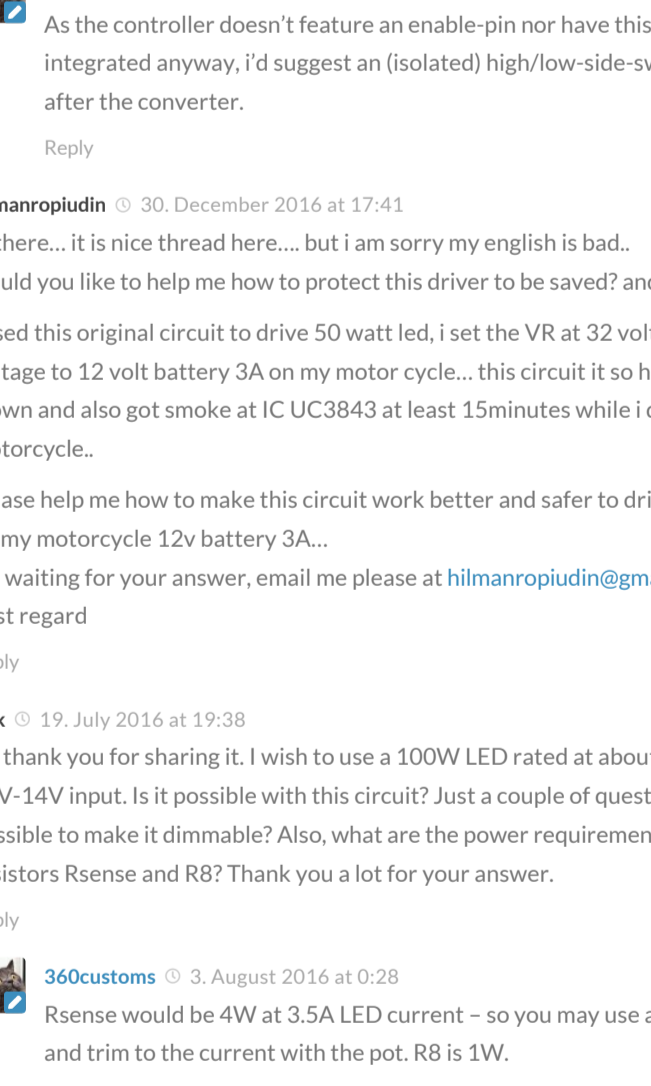

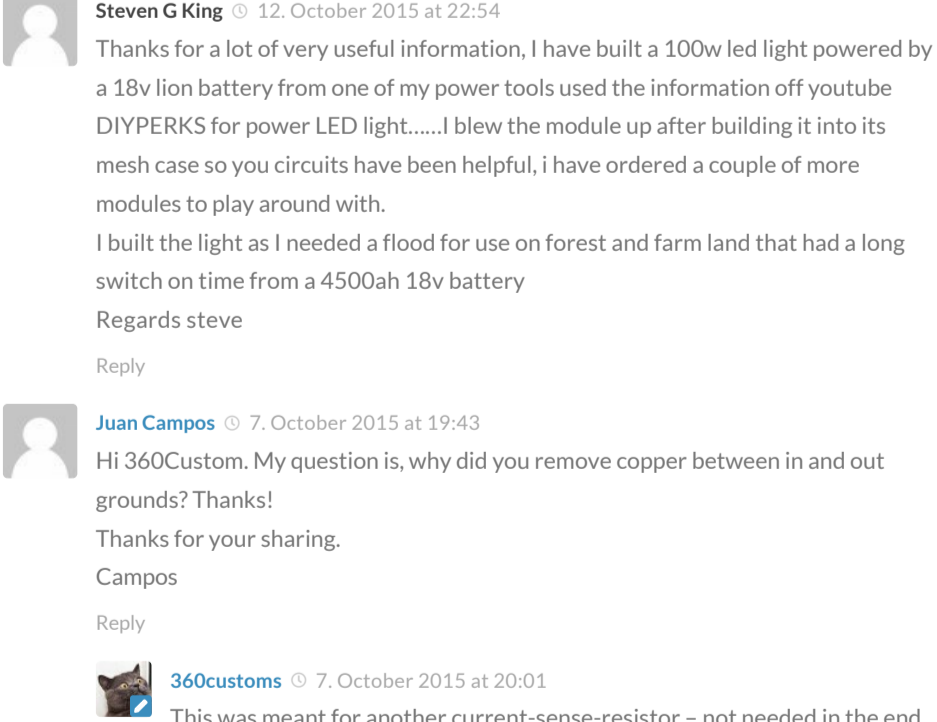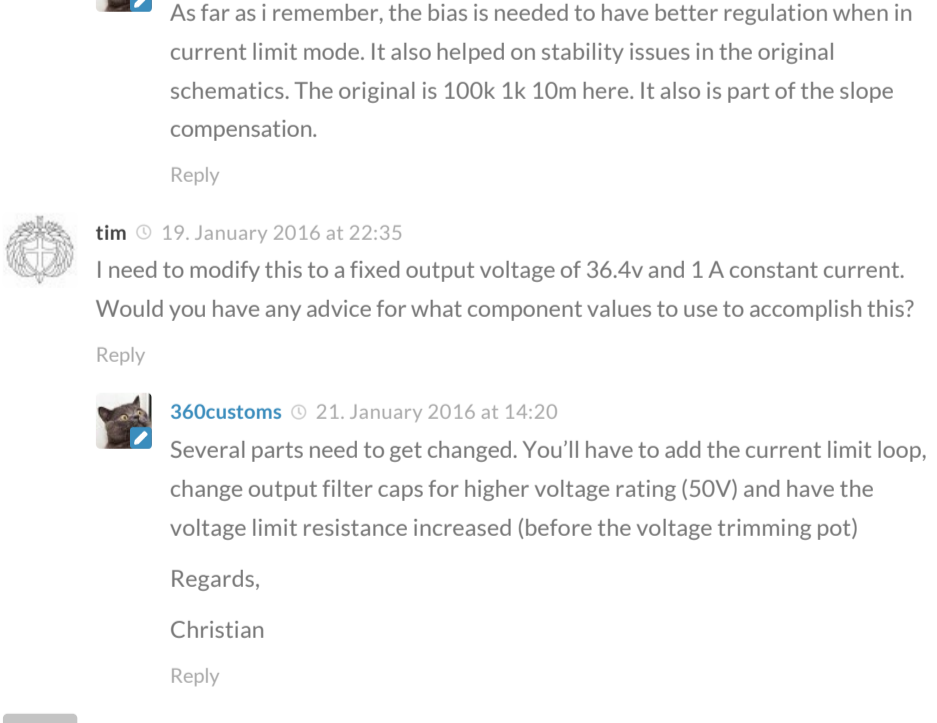Because the circuit with R8 (measuring shunt 10 mohm) is a bit on the low end, it is, to replace it with 50mOhm. This results in a higher control loop stability, also the feedback (compensation) to be interpreted high-ohm. The changes for constant voltage/constant current shown below:



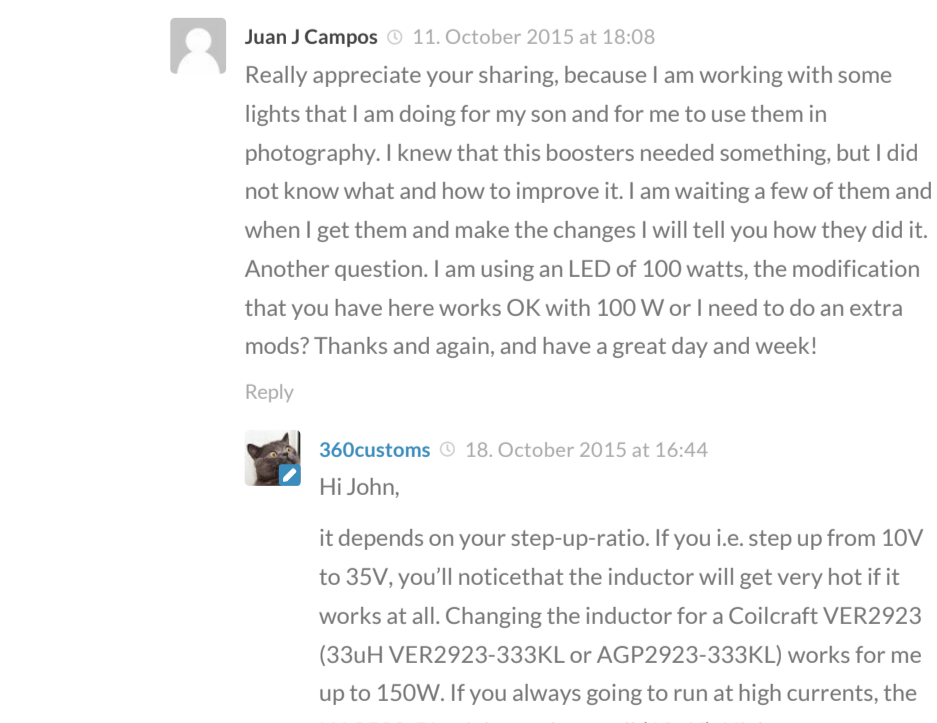Finally some pictures of the shutter speed on each fixed white balance (daylight) / Aperture of the shutter speed (separately for both subjects):



Upgrade

For great Step-Up ratios, it has proven to replace the coil against models from Coilcraft. Without further alteration, 33uH work here without any significant heating - even at 12V->36V and 150W power consumption. Coilcraft VER2923-333KL or AGP2923-333KL Coilcraft AGP2923-333KL

If voltage ripple is not an issue, Coilcraft HA3588-BL could be used.

If you would like to know more, look in the D amp Forum over.

LTSpice simulation: Download (zip)

Tags: AGP2923, Boost, CV, Coilcraft, Constant Current, HA3588, Konstantstromquelle, LED

Step Up: UC3842, UC3843, UC3843A, VER2923

PREVIOUS STORY: Upper surface roughness of a 250 GB platters

NEXT STORY: 18650 battery tank (mobile battery)

YOU MAY SO LIKE...

- TPA3250D2 - 2 x 70W Stereo Class-D Verstärker 18. DECEMBER 2015
- TPA3251D2 - 2 x 170W Stereo 350W Mono 189W Mono Class-D Verstärker 20. JULY 2015
- TPA3255 - 2 x 325W Stereo 600W Mono Class-D Verstärker 14. MARCH 2016

20 RESPONSES

Comments 19 | Pingbacks 1

Roman @ 11 October 2018 at 9:37
Hello,
nice design indeed, could you give a couple of tips how to apply the control function correctly in your design, for example apply the opto-coupling (fod817) & have possibility to switch ON/OFF the driver by MCU?
Thanks an advance for reply,
Roman,
Reply

360Customs @ 13 October 2018 at 14:34
As the controller doesn't feature an enable pin nor have this functionality integrated anyway, I'd suggest an (isolated) high/low-side switch in front of or after the converter.
Reply

hilmanropiudin @ 30 December 2014 at 17:41
hi there... it is nice thread here... but i am sorry my english is bad... would you like to help me how to protect this driver to be saved? and not very hot? i used this original circuit to drive 50 watt led, i set the VR at 32 volt... source input voltage to 12 volt battery 3A on my motor cycle... this circuit it so hot and was blown and also got smoke at IC UC3843 at least 15 minutes while i driven the motorcycle.
please help me how to make this circuit work better and safer to drive 50Watt led on my motorcycle 12v battery 3A...
i'm waiting for your answer, email me please at hilmanropiudin@gmail.com
best regard
Reply

Mik @ 19 July 2014 at 19:38
Hi, thank you for sharing it. I wish to use a 100W LED rated at about 35V, using 12V-14V input. Is it possible with this circuit? Just a couple of questions more: it is possible to make it dimmable? Also, what are the power requirements for the resistors Rsense and R8? Thank you a lot for your answer.
Reply

360Customs @ 3 August 2016 at 0:28
Rsense would be 4W at 3.5A LED current - so you may use a smaller value and trim to the current with the pot. R8 is 1W.
Reply

Matt090 @ 20 May 2016 at 20:53
Hi, thanks for this post!
Even if im a bit late these DC boosters are still the same and i learned a bit more on how they work
Can i ask what's the meaning of R99 on this circuit? why would you need to give a constant bias to ISENSE? Also why do you use 9V for the voltage regulated one and the Vref for constant-current one?
thanks,
Reply

360Customs @ 19 June 2016 at 23:34
As far as i remember, the bias is needed to have better regulation when in current limit mode. It also helped on stability issues in the original schematics. The original is 100k 1k 10m here. It also is part of the slope compensation.
Reply

tim @ 19 January 2016 at 22:35
I need to modify this to a fixed output voltage of 36.4v and 1A constant current. Would you have any advice for what component values to use to accomplish this?
Reply

360Customs @ 21 January 2016 at 14:20
Several parts need to get changed. You'll have to add the current limit loop, change output filter caps for higher voltage rating (50V) and have the voltage limit resistance increased (before the voltage trimming pot)
Regards,
Christian
Reply

Steven G King @ 12 October 2015 at 22:54
Thanks for a lot of very useful information, I have built a 100w led light powered by a 18v lion battery from one of my power tools used the information off youtube DIVERKES for power LED light..... I blew the module up after building it into its mesh case so your circuits have been helpful, I have ordered a couple of more modules to play around with.
I built the light as i needed a flood for use on forest and farm land that had a long switch on time from a 4500ah 18v battery
Regards steve
Reply

Juan Campos @ 7 October 2015 at 19:43
Hi 360Custom. My question is, why did you remove copper between in and out grounds? Thank!
Thanks for your sharing.
Campos
Reply

360Customs @ 7 October 2015 at 20:01
This was meant for another current-sense-resistor - not needed in the end. Btw, if you change the inductor for a Coilcraft VER2923 (10-33uH) the converter does the full 150W with ease, even big boost-ratios of >1:3 (i.e. 10V -> 35V).
Regatta Christian
Reply

Juan J Campos @ 11 October 2015 at 18:08
Really appreciate your sharing, because I am working with some lights that I am doing for my son and for me to use them in photography. I know that this boosters needed something, but I did not know what and how to improve it. I am waiting a few of them and when I get them and make the changes I will tell you how they did it. Another question, I am using an LED of 100 watts, the modification that you have here works OK with 100 W or I need to do an extra mods? Thanks and again, and have a great day and week!
Reply

360Customs @ 18 October 2015 at 16:44
Hi John,
it depends on your step-up ratio. If you i.e. step up from 10V to 35V, you'll notice that the inductor will get very hot if it works at all. Changing the inductor for a Coilcraft VER2923 (33uH VER2923-333KL or AGP2923-333KL) works for me up to 150W. If you always going to run at high currents, the HA3588-BL might work as well (10uH). Higher current -> less inductance needed (but higher ripple).
Regards, Christian
Reply

Mike @ 24 March 2015 at 19:14
Hello,
Thank you for this interesting designs, they offer a wonderful base for further projects
A small discrepancy I noticed though:
Considering the Spice circuits to the constant current and the summary is marked in colour, diode D2/D3 is wired differently. The spice is right behind the potentiometer VR1/R3 and influenced both FB direct_COMP via R1 and the VR2. The shimmery plan is the diode directly before FB, before VR2 come on in, and * behind * R1(R20) is to COMP.
It will vote because exists but the typical voltage drop of the diode, only a version, I suppose.
Is it correct to take the Spice version here?
Best regards!
Mike
Reply

360Customs @ 6 April 2015 at 17:49
Hi Mike,
Thanks for the comments. Both circuits are equivalent to the circuit of R1 at COMP. Both will work - the SPICE circuit is preferable. (Theoretically push the diode to the voltage divider, then it will be shown)
Greeting Christian
Reply

Thiago @ 22 November 2014 at 21:13
Hello, congratulations on your posting.
I have convert identical. I want to use in electric motor 18 VDC x 8A through the 12 volt battery.
What change in this circuit that could help me.
Return wait.
Thank you!
Reply

360Customs @ 23 November 2014 at 11:53 am
18VDC * 8A 144VA - way - to much for the converter. You'd better got for a 600W converter that can be found on eBay at ~ \$14.
Regards, Christian
Reply

Max @ 17 July 2014 at 1:48
Get them here: <http://www.ebay.de/itm/310523503559>
Reply

LEAVE A REPLY

Comment

* Check box GDPR is required. This form collects your name, email and content so that we can keep track of the comments placed on the website. For more info check our privacy policy where you'll get more info on where, how and why we store your data. I agree

Name * Email *

Website

Save my name, email, and website in this browser for the next time I comment.