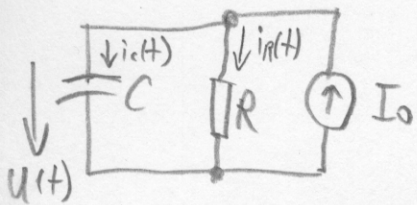


# Leichte Aufgabe



$$I_0 = i_c(t) + i_R(t), \quad u(t) = R \cdot i_R(t) = R \cdot (I_0 - i_c(t))$$

$$i_c(t) = C \cdot \frac{du(t)}{dt}$$

$$i_c(t) = C \cdot \frac{d}{dt} (R \cdot I_0 - R \cdot i_c(t)) = C \frac{d}{dt} (R \cdot I_0) - RC \frac{di_c(t)}{dt}$$

$$i_c(t) = -RC \frac{di_c(t)}{dt} \leftarrow \text{GDE}$$

Ansatz:  $i_c(t) = A + B \cdot e^{\lambda t}$

Randbedingungen:  $i_c(t=0) = I_0 = A + B$

$$i_c(t \rightarrow \infty) = 0 = A \quad (\lambda < 0)$$

$$\Rightarrow A = 0, B = I_0$$

$$\Rightarrow i(t) = I_0 e^{\lambda t}$$

$$\frac{di(t)}{dt} = I_0 \lambda e^{\lambda t}$$

einsetzen in GDE  $\Rightarrow$

$$I_0 e^{\lambda t} = -RC \cdot I_0 \lambda e^{\lambda t}$$

$$\Rightarrow 1 = -RC \cdot \lambda$$

$$\Rightarrow \lambda = -\frac{1}{RC}$$

$$\Rightarrow i(t) = I_0 \cdot e^{-\frac{t}{RC}}$$

$$\text{und: } u(t) = R \cdot (I_0 - I_0 \cdot e^{-\frac{t}{RC}})$$

$$u(t) = R \cdot I_0 \cdot (1 - e^{-\frac{t}{RC}})$$

wichtig  $\rightarrow$

Bestimmen von R:

$$u(t_1) \stackrel{!}{=} U_1, \quad (t_1 = 60 \text{ms}, U_1 = 5 \text{V}, C = 47 \text{nF}, I_0 = 5 \mu\text{A})$$

⇓

$$U_1 = R \cdot I_0 \cdot \left(1 - e^{-\frac{t_1}{RC}}\right) = R \cdot I_0 - R \cdot I_0 \cdot e^{-\frac{t_1}{RC}}$$

$$R \cdot I_0 \cdot e^{-\frac{t_1}{RC}} = R \cdot I_0 - U_1$$

$$e^{-\frac{t_1}{RC}} = 1 - \frac{U_1}{R \cdot I_0}$$

$$\text{Substitution } x := \frac{1}{R} \Rightarrow e^{-\frac{t_1}{C} \cdot x} = 1 - \frac{U_1}{I_0} \cdot x$$

$$\alpha := \frac{t_1}{C}, \quad \beta := -\frac{U_1}{I_0}$$

$$e^{-\alpha x} = 1 + \beta \cdot x$$

$$\cancel{\beta \cdot x} \quad \gamma := \frac{-1}{\beta} = +\frac{I_0}{U_1}$$

$$\Rightarrow e^{-\alpha x} = -\gamma \cdot \beta + \beta \cdot x = \beta \cdot (x - \gamma)$$

(Wikipedia)

$$\Rightarrow x = \gamma + \frac{1}{\alpha} \cdot \text{Wo} \left( \frac{\alpha}{\beta} e^{-\alpha \cdot \gamma} \right) = \frac{1}{R}$$

$$\Rightarrow R = \frac{1}{\frac{I_0}{U_1} + \frac{C}{t_1} \cdot \text{Wo} \left( -\frac{t_1}{C} \cdot \frac{I_0}{U_1} \cdot e^{-\frac{t_1}{C} \cdot \frac{I_0}{U_1}} \right)}$$

Lambertsche W-Funktion!