
By Wes Hayward (W7ZOI)

TriQuint Semiconductor
Beaverton, Oregon

**Introduction
to Radio
Frequency Design**

Copyright © 1994 by
The American Radio Relay League, Inc.

Copyright secured under the Pan-American
Convention.

This work is publication number 191 of the Radio
Amateur's Library, published by the League. All
rights reserved. No part of this work may be
reproduced in any form except by written
permission of the publisher. All rights of
translation are reserved.

Quedan reservados todos los derechos.

ISBN: 0-87259-492-0

First ARRL Edition

Contents

PREFACE	ix
1 LOW FREQUENCY TRANSISTOR MODELS	1
1.1 Introduction: Basic Models	1
1.2 Small-Signal Models for the Bipolar Transistor	3
1.3 Biasing and Bypassing the Bipolar Transistor	10
1.4 Large-Signal Operation of the Bipolar Transistor	14
1.5 Gain, Power, and Negative Feedback	18
1.6 Modeling the Field-Effect Transistor	26
References	30
Suggested Additional Readings	30
2 FILTER BASICS	32
2.1 Network Analysis in the Time Domain	33
2.2 Network Analysis in the Frequency Domain	36
2.3 Poles, Zeros, and the Series Tuned Circuit	39
2.4 Filter Concepts	44
2.5 The Ladder Method	51
2.6 Losses in Reactive Components and Quality Factor	54
2.7 The All-Pole Low Pass Filter	59

2.8	Filter Denormalization, Practical Low Pass, High Pass, and Bandpass Structures	68
	References	73
3	COUPLED RESONATOR FILTERS	75
3.1	Impedance Transforming Networks	75
3.2	Normalized Coupling and Loading Coefficients	82
3.3	The Double Tuned Circuit	90
3.4	Experimental Methods, The Dishal Technique	95
3.5	Quartz Crystal Filters	101
	References	108
4	TRANSMISSION LINES	109
4.1	Transmission Line Fundamentals	110
4.2	The Voltage Reflection Coefficient and Standing Waves	115
4.3	The Smith Chart and Its Applications	121
4.4	Practical Transmission Lines	132
4.5	Impedance Transforming Networks	137
4.6	Transmission Line Measurements	151
	References	159
	Suggested Additional Readings	160
5	TWO-PORT NETWORKS	161
5.1	Two-Port Network Fundamentals	161
5.2	Interconnection of Two-Port Networks	168
5.3	The Hybrid-Pi Transistor Model	172
5.4	Amplifier Design with Admittance Parameters	176
5.5	Design Examples with Admittance Parameters	183
5.6	Scattering Parameters	191
	References	201
	Suggested Additional Readings	201
6	PRACTICAL AMPLIFIERS AND MIXERS	202
6.1	Noise in Amplifiers	202
6.2	Noise Models and Noise Matching	210
6.3	Distortion in Amplifiers and the Intercept Concept	219
6.4	Mixers	232
6.5	Intermediate Frequency Amplifiers	246

References 259
Suggested Additional Readings 259

7 OSCILLATORS AND FREQUENCY SYNTHESIZERS 261

7.1 Oscillator Concepts 262
7.2 The Colpitts Oscillator 265
7.3 Further *LC* Oscillator Topics 279
7.4 Crystal Controlled Oscillators 286
7.5 Noise in Oscillators 292
7.6 Negative Resistance Oscillators 301
7.7 Methods of Frequency Synthesis 311
7.8 Phase-Locked Loop Frequency Synthesis 323
7.9 Voltage Controlled Oscillators and Improved Synthesizers 330
References 338
Suggested Additional Readings 339

8 THE RECEIVER: AN RF SYSTEM 341

8.1 Receiving Systems 342
8.2 Receiver Evaluation and Measurements 349
8.3 Intermediate Frequency Amplifier Systems and Gain Control 356
8.4 Front-End Design 367
References 372
Suggested Additional Readings 372

INDEX 373