

# Design and Fabrication of High-Fidelity Vacuum Tube Audio-Frequency Power Amplifiers

---

Gregory L. Charvat, **by**

for  
MIT Haystack Observatory Open Lunch  
February 3, 2010

**Danger: Do not attempt to build anything shown here unless you are experienced and trained in working with high voltage**

# Vacuum Tube Audio


- \* Vacuum tube sound
- \* musicians prefer it
- \* High peak power
- \* Vintage appearance



(vacuum tube home theater system)

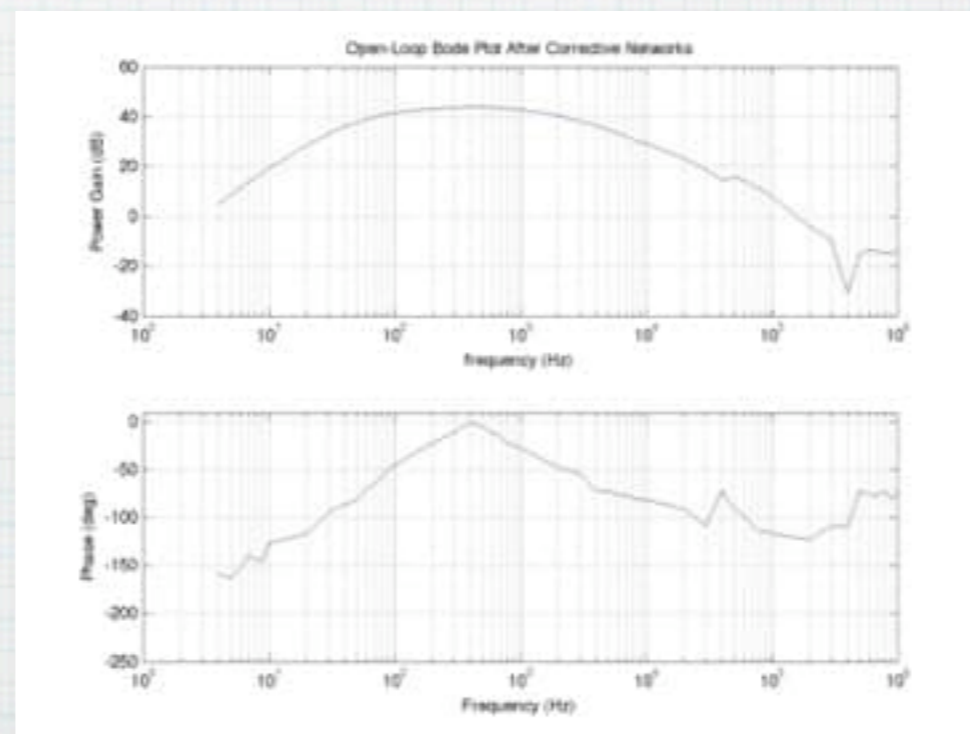
# Outline

- \* Simple vacuum tube pre-amplifier
- \* Tube power amplifier philosophy
- \* Class AB power amplifier
- \* Summary



# Build this Simple Pre-Amplifier

2 Channel  
25 dB Gain

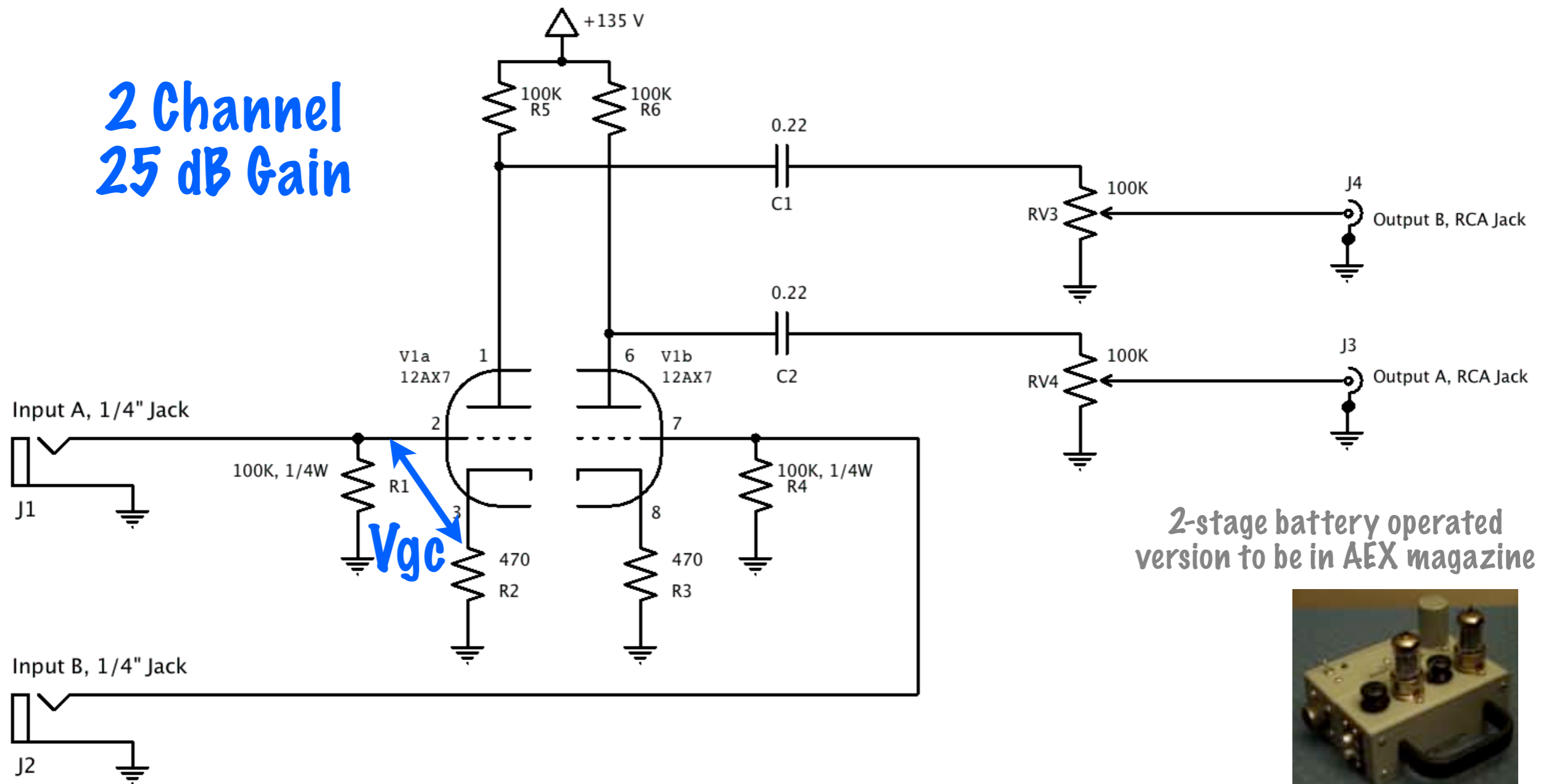


- \* Triodes are similar to N-channel J-FETs, except they are always negative biased w.r.t. the cathode ( $V_{gc} < 0 V$ )
- \* biasing is easily achieved by using a cathode resistor

# Tube Power Amplifier Design Philosophy


- \* Time domain audio signal:
  - \* low average power relative to peaks
  - \* low duty cycle of peaks (depending on type of music)
- \* Ideally suited for power amplification by vacuum tubes

Peak →  
RMS Average →

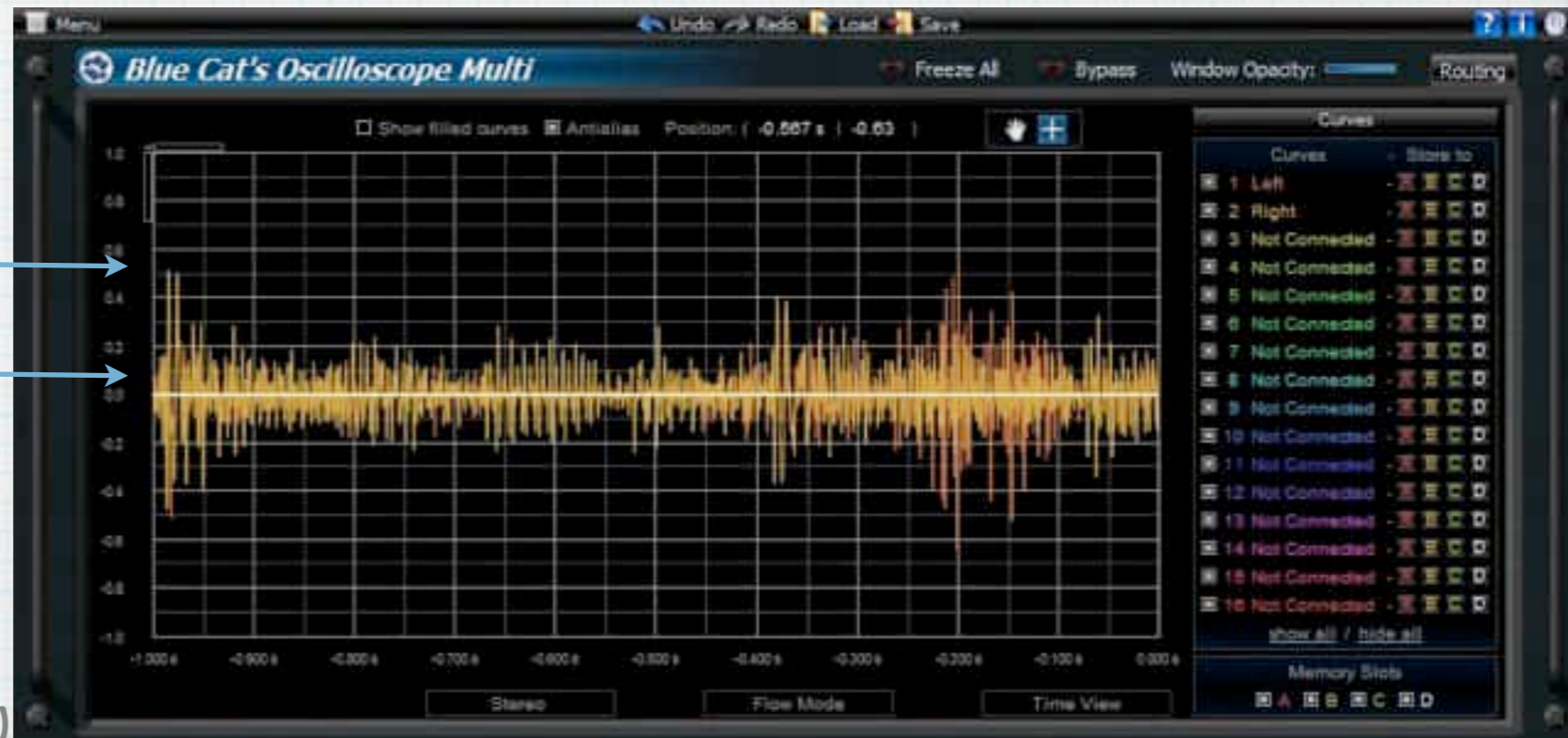

(time domain of music image from Blue Cat Audio)

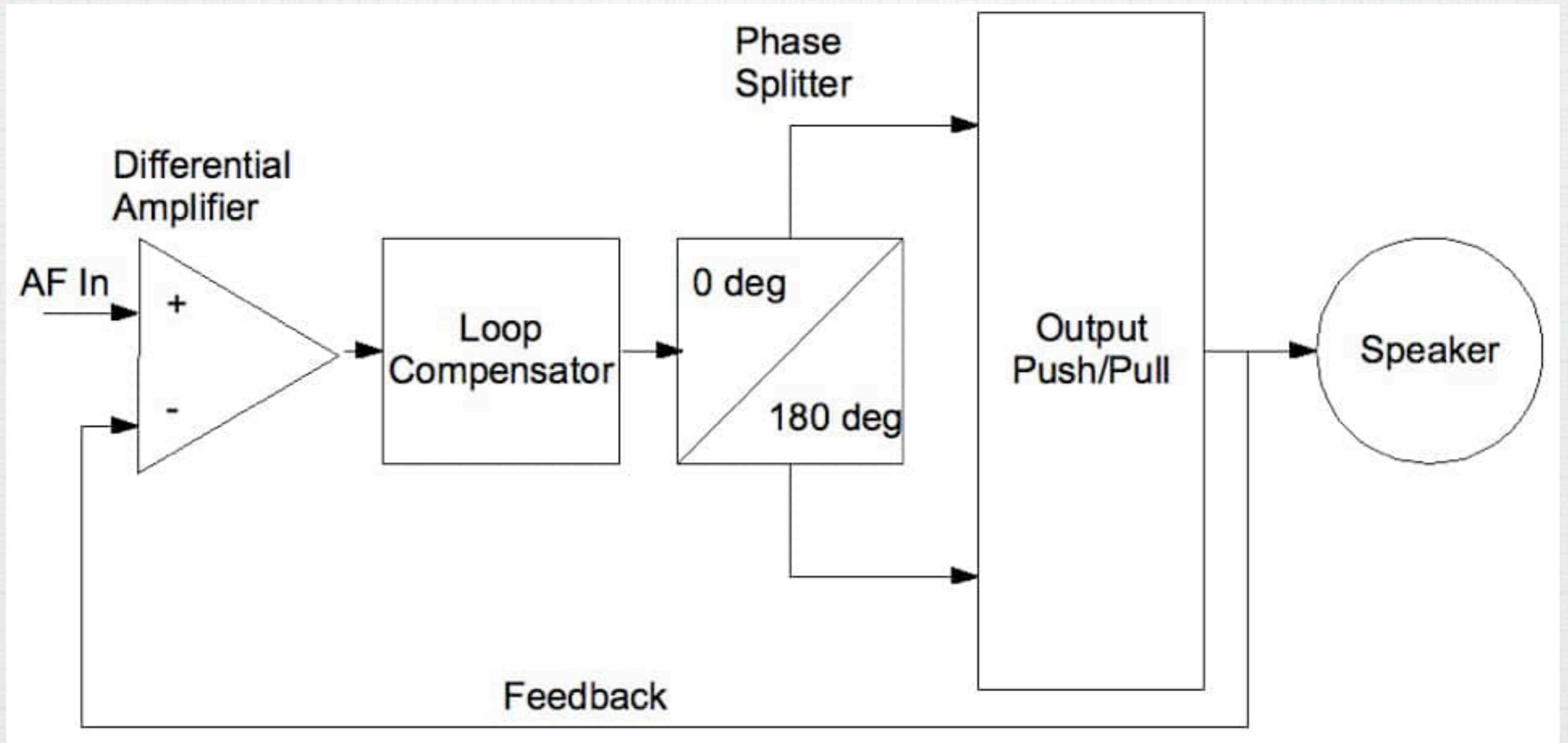
# Block Diagram: Class AB Power Amplifier



# Design Procedure

1. Construct power supply
2. Make output
3. Design phase splitter
4. Build differential amplifier
5. Measure open-loop frequency response
6. Design loop compensator
7. Re-measure open-loop and closed-loop response
8. Done!

# Construct the Power Supply

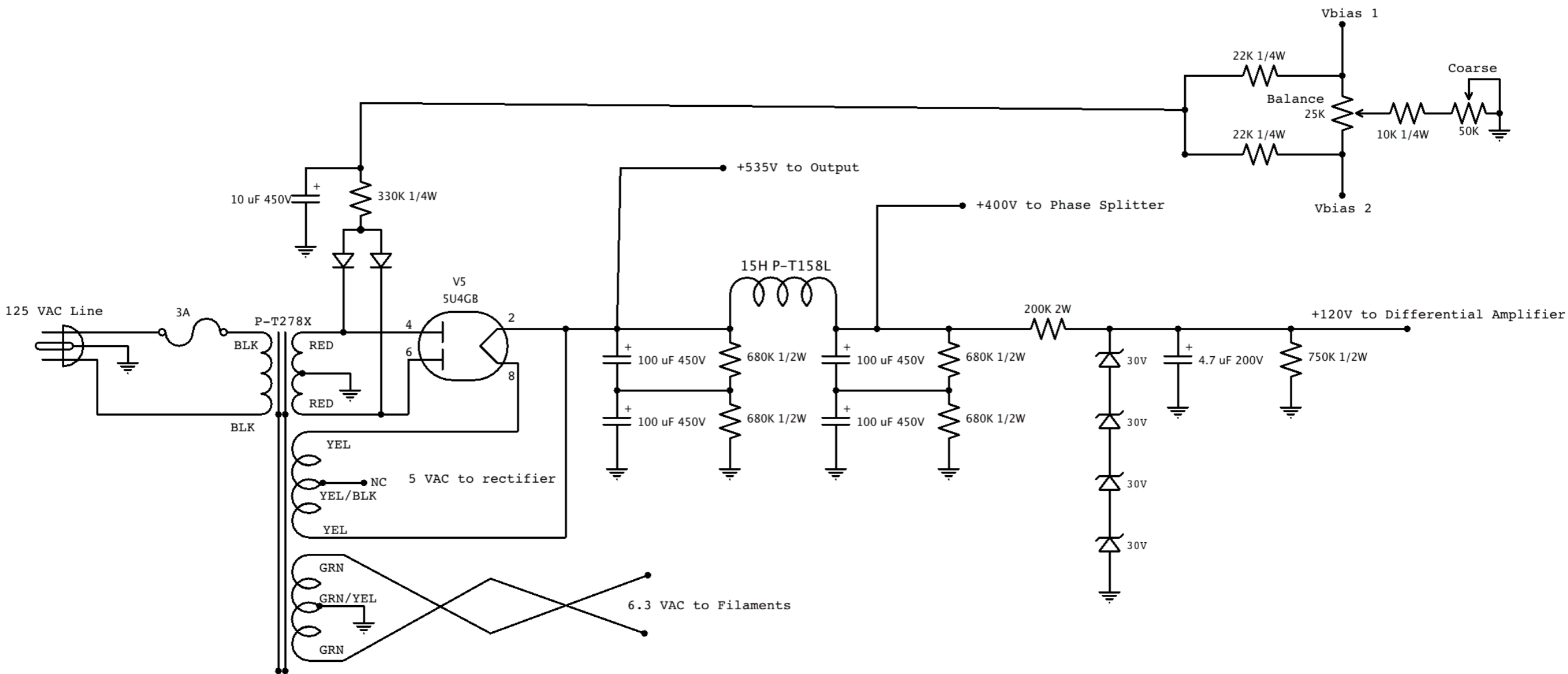


- \* Isolates each stage
- \* (or else oscillation will occur)
- \* Provides direct bias



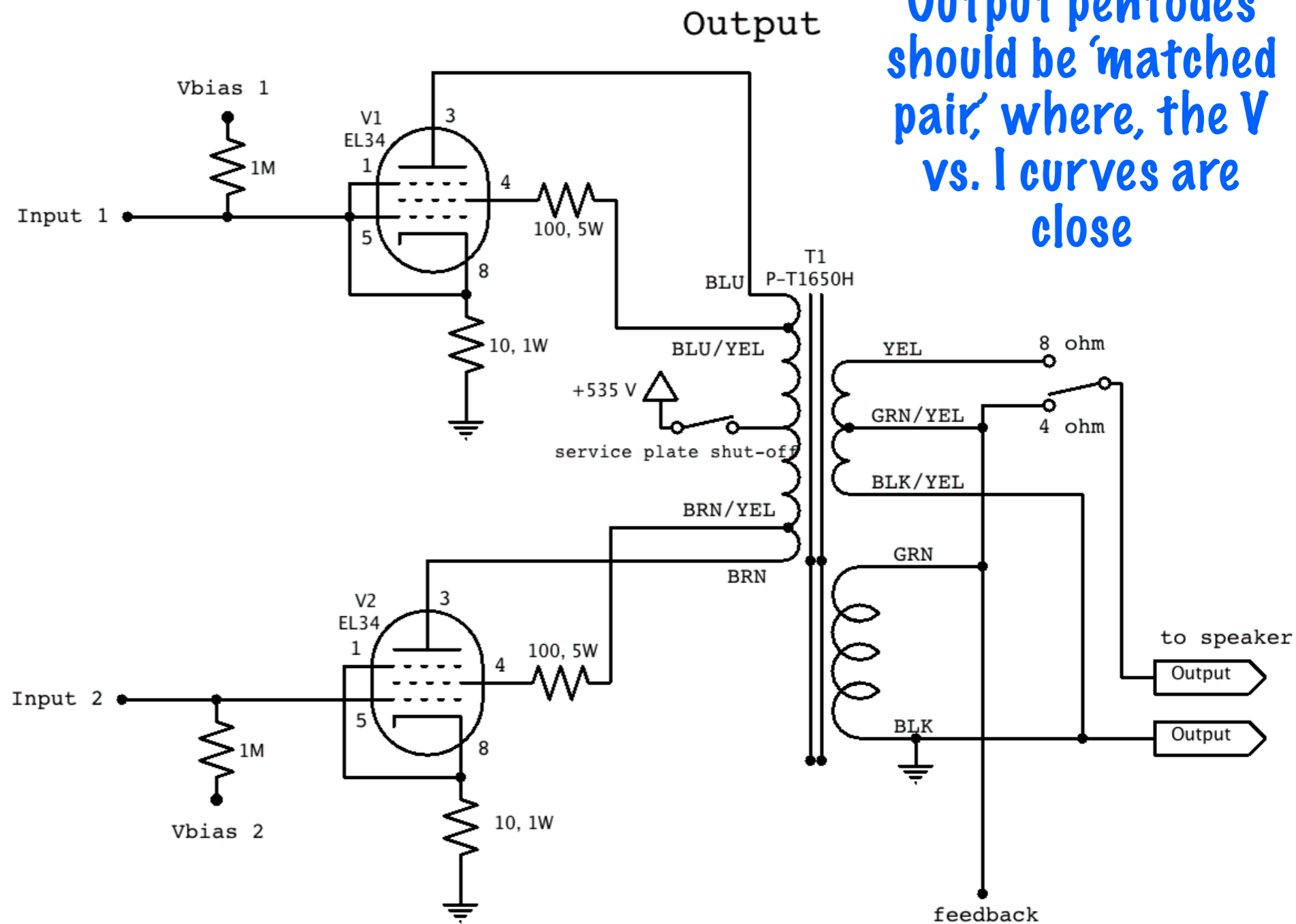
# Make the Push-Pull Output

- \* Follow data sheets
- \* Direct bias utilized here, however, cathode bias is **STRONGLY RECOMMENDED**
- \* Quiescent current = 60 mA for class AB, 25 mA for class B



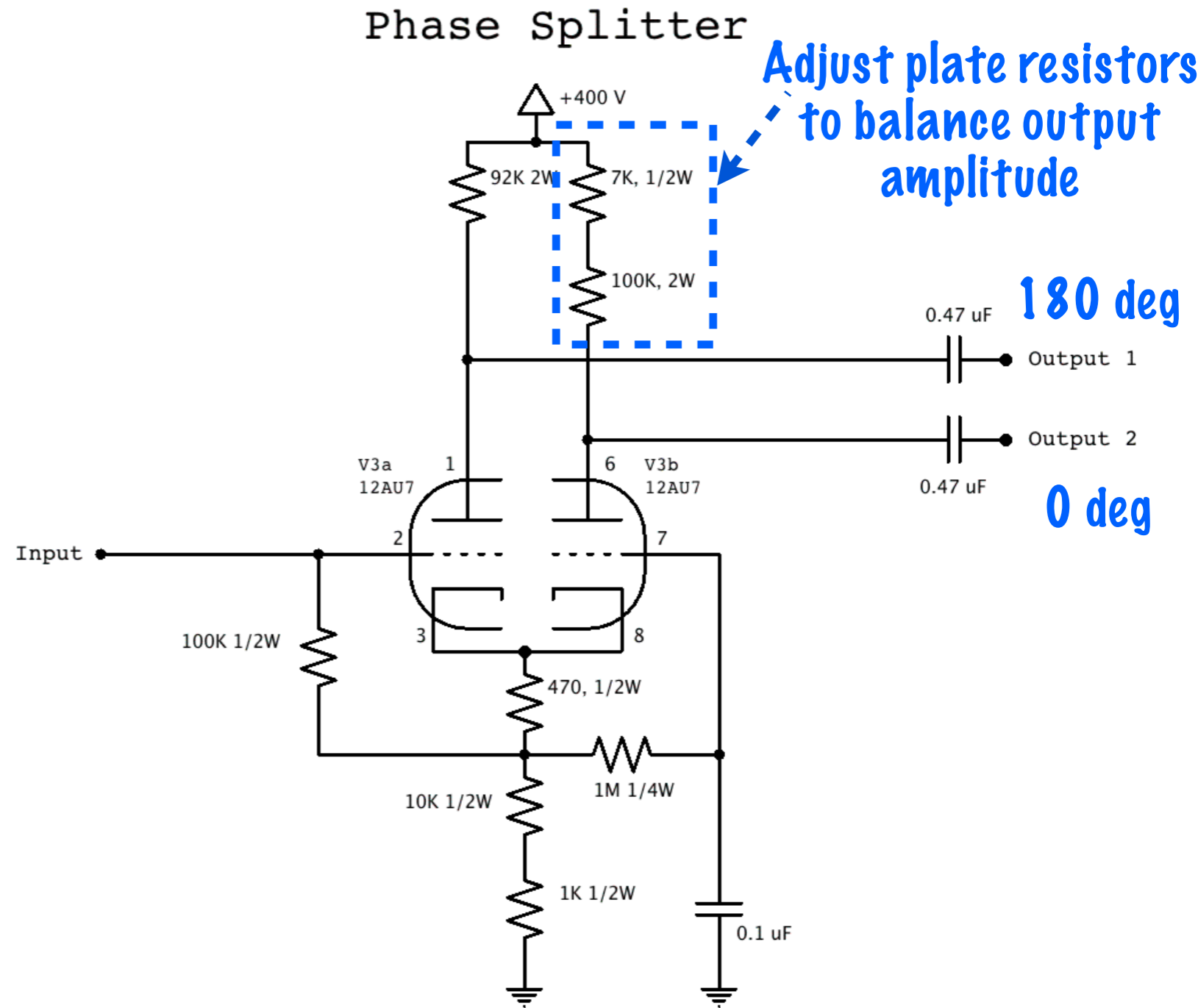
# Design a Phase Splitter

- \* Provides 0/180 deg split to drive push-pull output
- \* This version provides large output swing and forward loop gain
- \* Balance gain by adjusting plate resistors




# Build the Differential Amplifier

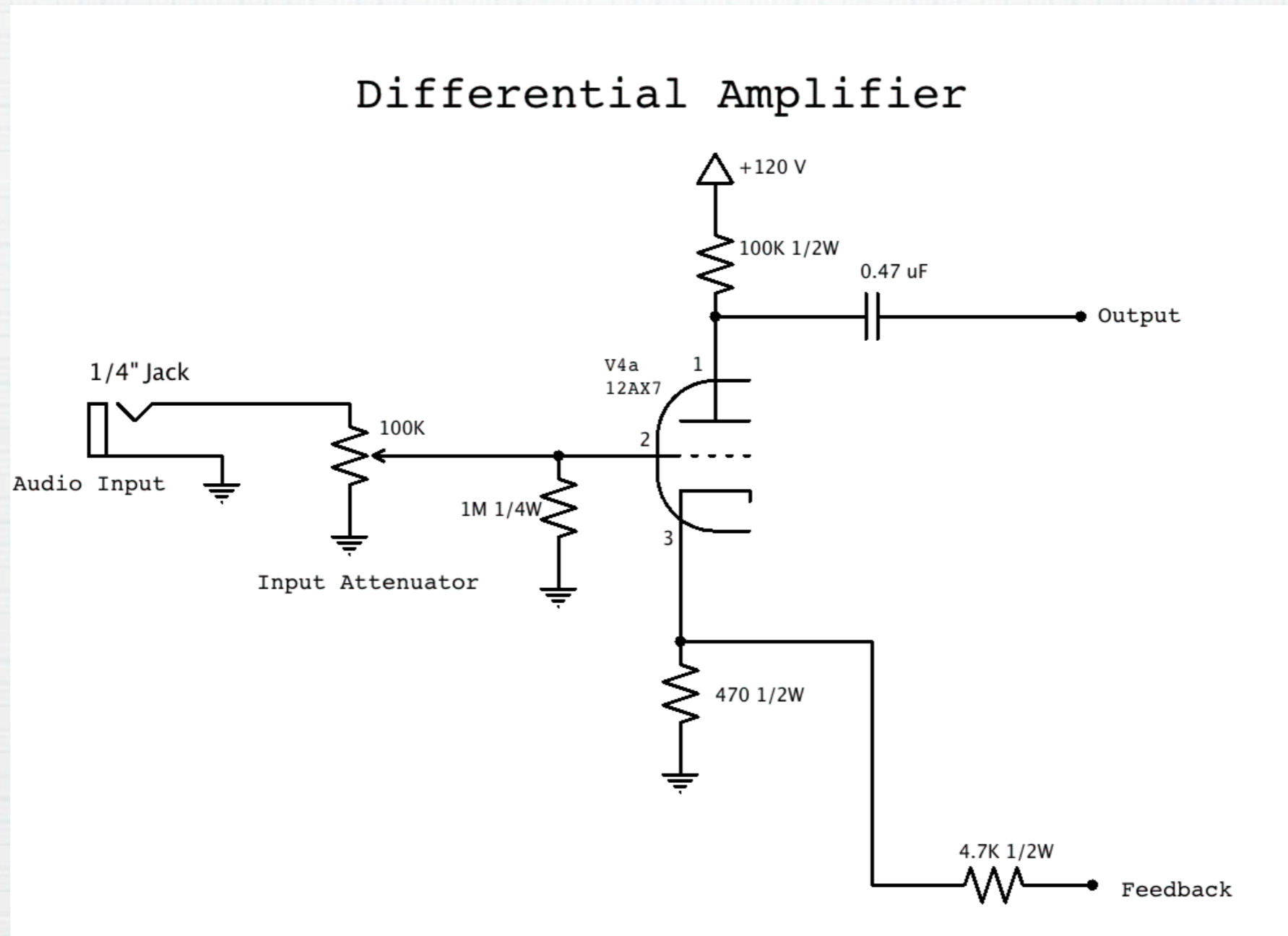

- \* Similar to the simple pre-amp
- \* Provides the majority of forward loop gain
- \* Closes feedback loop
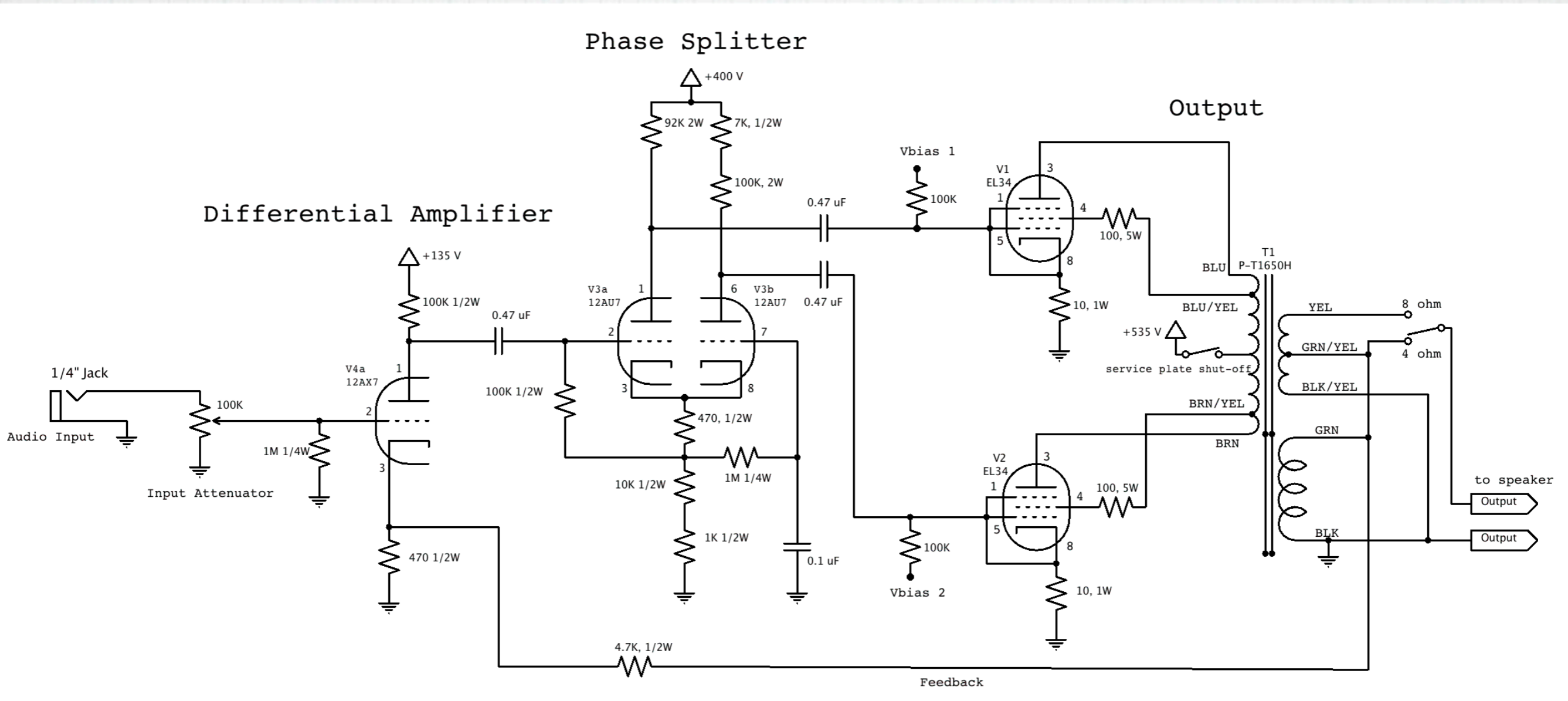
# Complete circuit (but not compensated yet!)



Warning: this will oscillate






Power Supply

Diff. Amp

Phase Splitter

Output

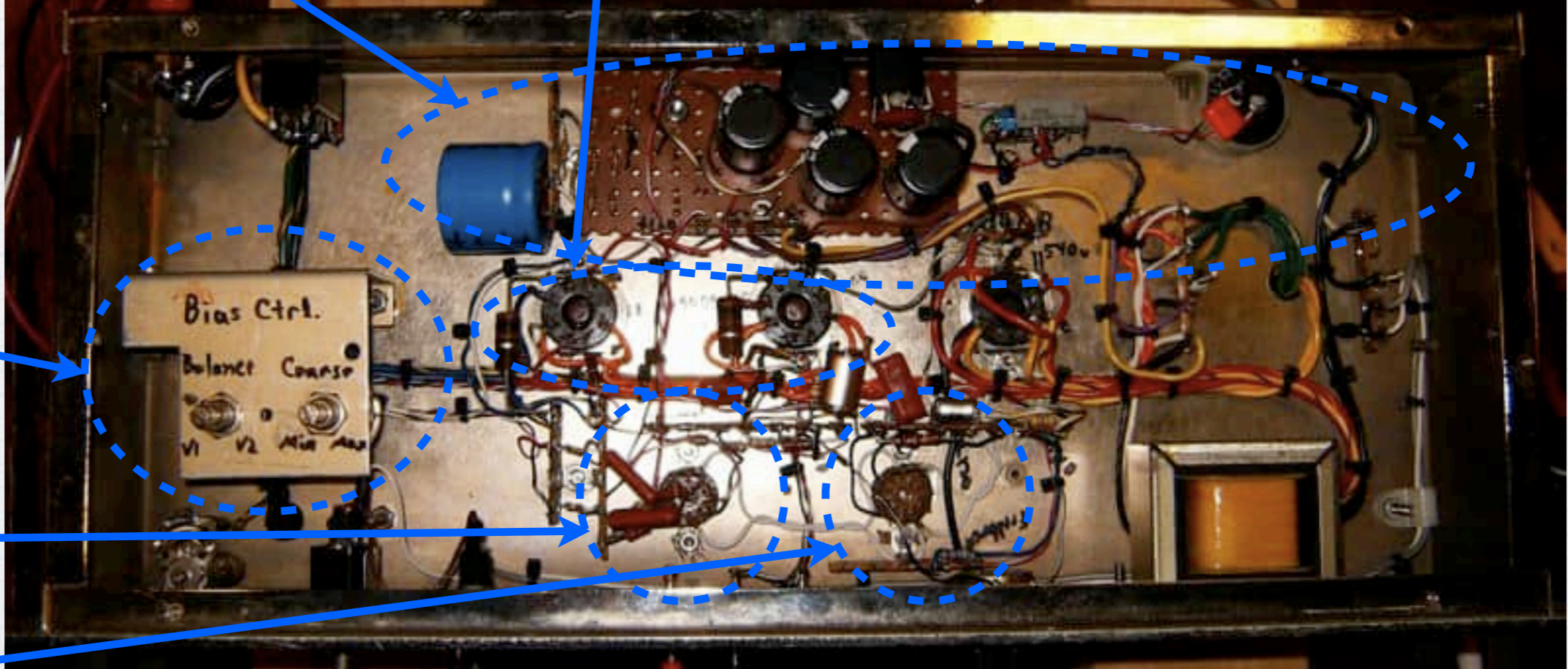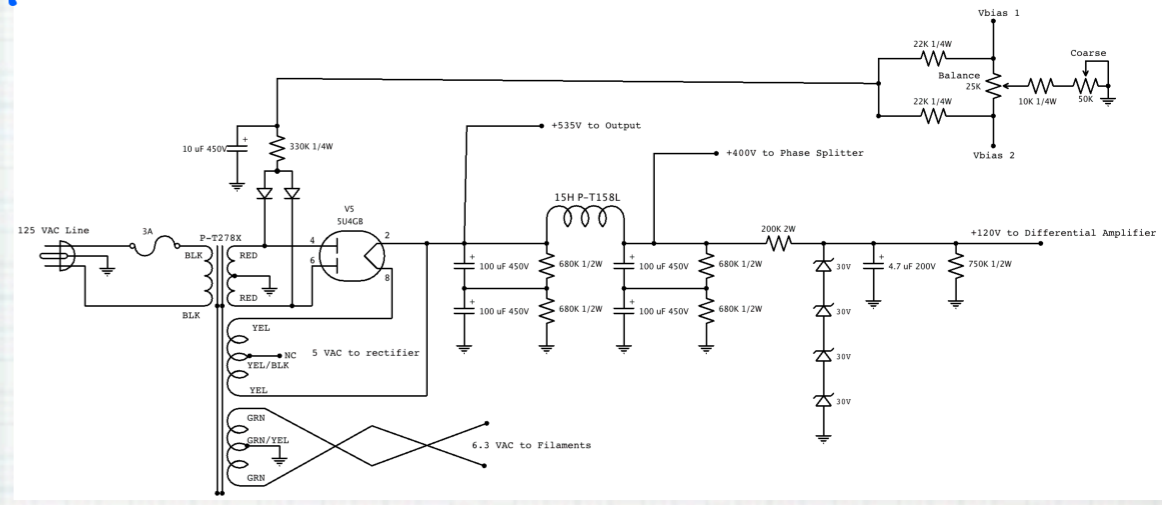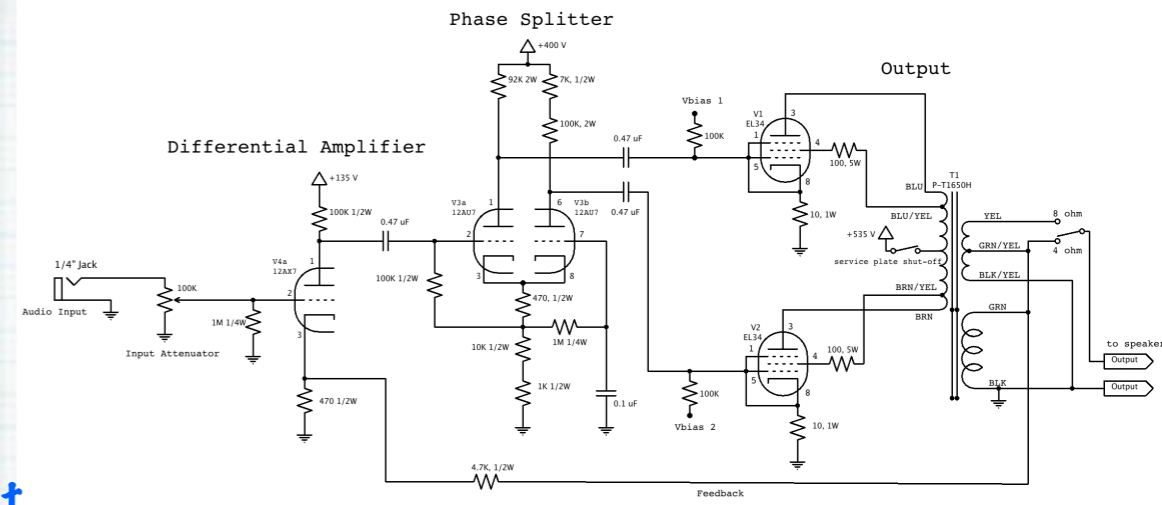


Bias

Phase Splitter

Diff. Amp
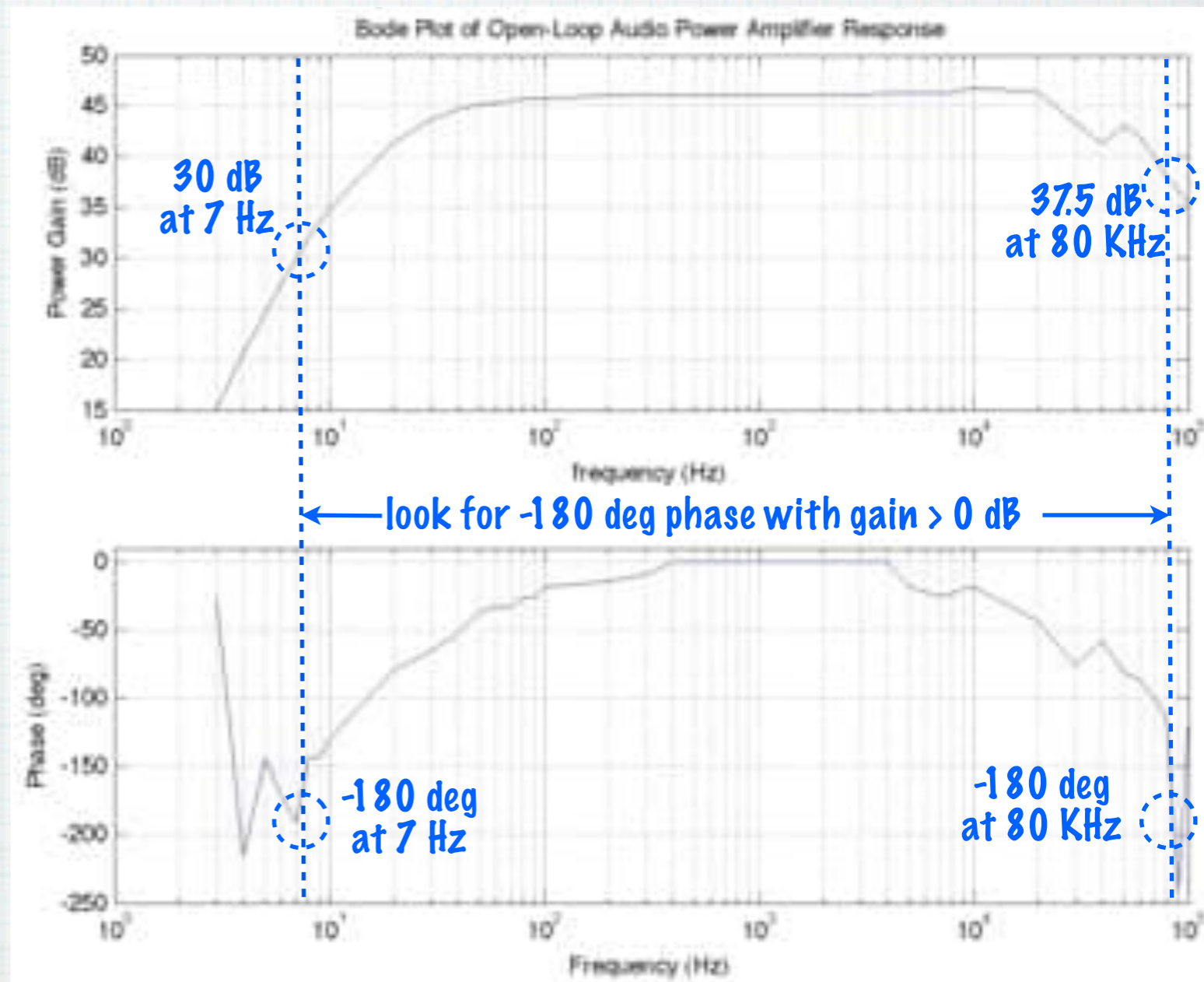
# Measure the Open-Loop Transfer Function using a Bode Plot




- \* temporarily remove the feedback resistor
- \* measure in decades (1-10, 100-1K, 10K-100K, 100K-300K)
- \* magnitude (dB relative) =  $20 \cdot \log_{10}(V_{out}/V_{in})$  with 8 ohm load at output
- \* phase (deg) =  $360 \cdot \text{frequency} \cdot \text{tdelay\_between\_peaks}$

# Design a Loop Compensator

- \* Preferred method: Learned, V. "Corrective networks for feedback circuits," Proc. I.R.E. 32.7, (July 1944), 403.
- \* attenuation and phase slopes to reduce gain and control phase
- \* developed for placement between tube stages
- \* summarized in: F. Langford-Smith, Radio Designer's Handbook 4th Ed., Reed Educational and Professional Publishing Ltd, London, 1997, pp. 369-371.
- \* Matlab program [www.mit.edu/~gr20603](http://www.mit.edu/~gr20603) click on 'Quad Tube Amplifier', scroll down and click on 'Bode plots and loop compensation network calculations using matlab'
- \* manually enter high and low frequencies just before -180 deg
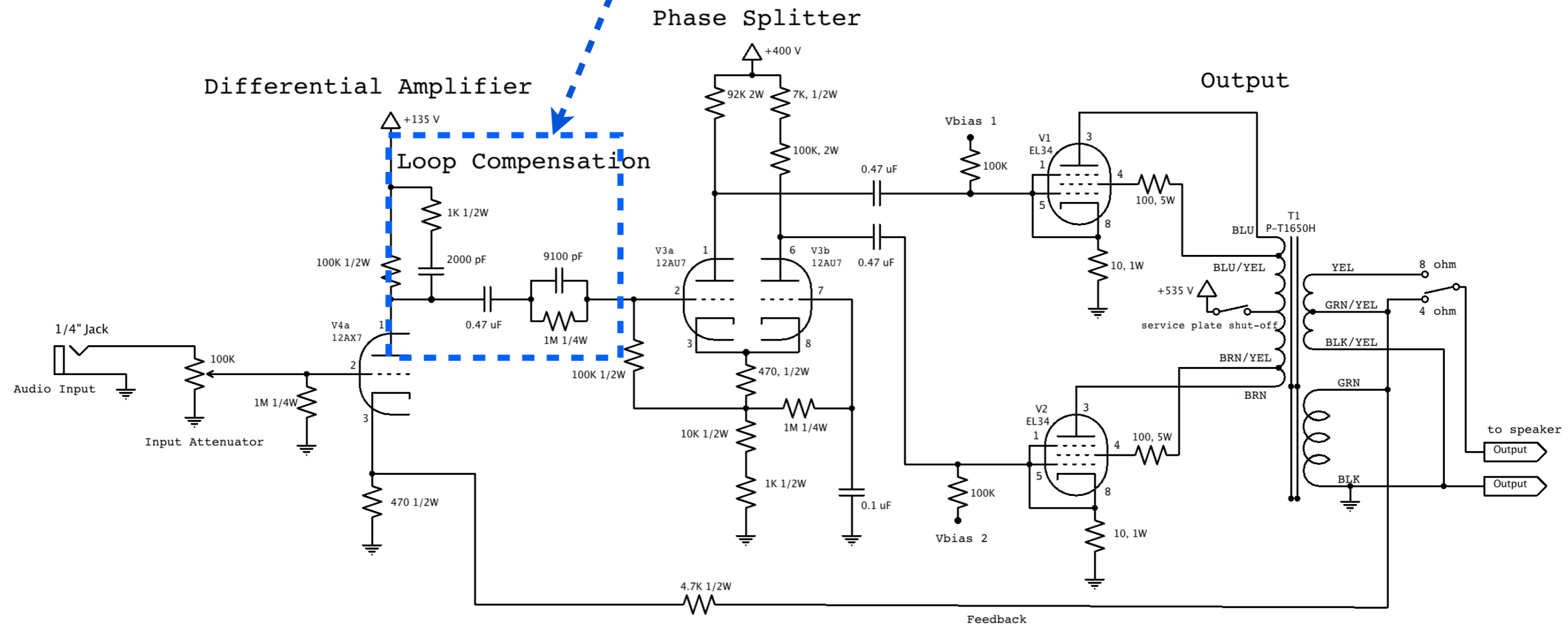
# Install Compensation Circuit Between Diff Amp. and Phase Splitter






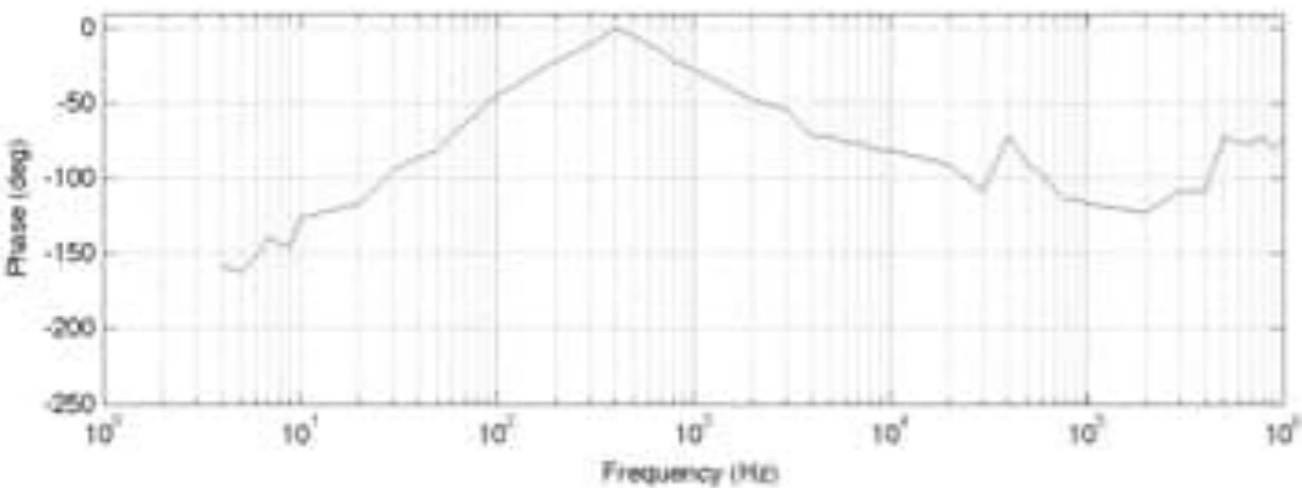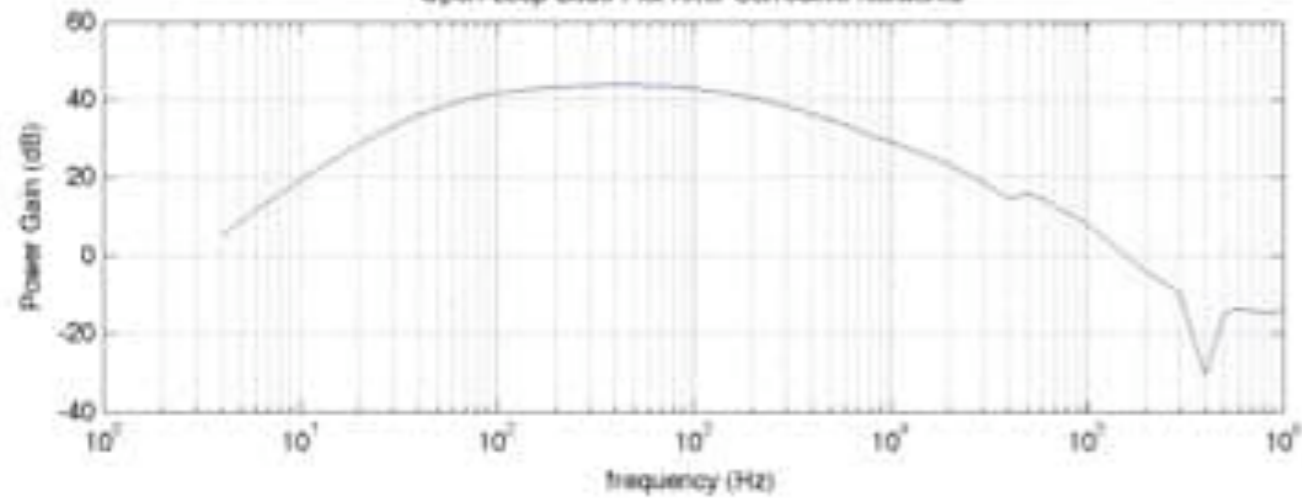
# Re-Plot to Verify Stability and Measure Performance



phase  $> -180$  deg everywhere there is gain  $> 0$  dB

Open-Loop Bode Plot After Corrective Networks



Open-Loop  
Transfer Function

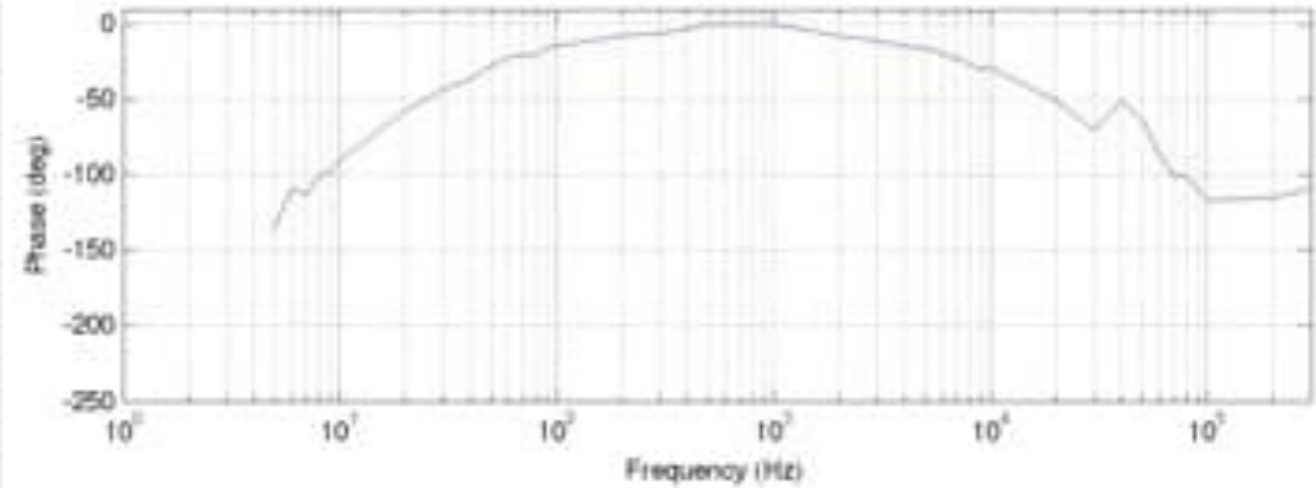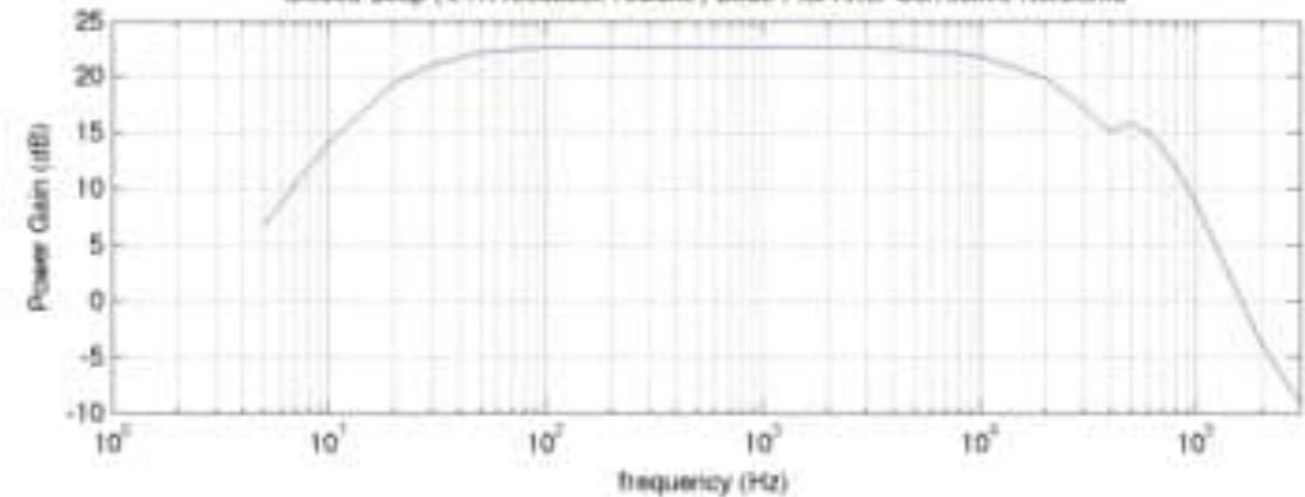Closed-Loop (4.7k feedback resistor) Bode Plot After Corrective Networks




Closed-Loop  
Transfer Function

**Now you are ready to rock!**
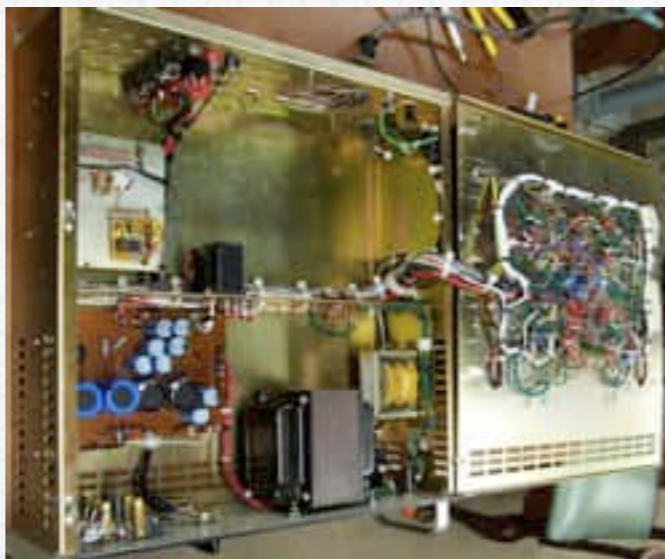
# Performance

- \* 480 watts peak power output/ch
- \* 0.45 % THD at 1 KHz
- \* 20 Hz - 25 KHz BW
- \* 4 channel amplifier



- \* 293.7 watts peak power output
- \* 0.65 % THD at 1 KHz
- \* 10 Hz - 25 KHz
- \* single-channel amplifier



# Summary

- \* Simple pre-amp shown
- \* Power-Amp design procedure
- \* Resources:
  - \* Radio Designer's Handbook
  - \* Audio Express Magazine
  - \* [gregory.charvat@ll.mit.edu](mailto:gregory.charvat@ll.mit.edu)

