
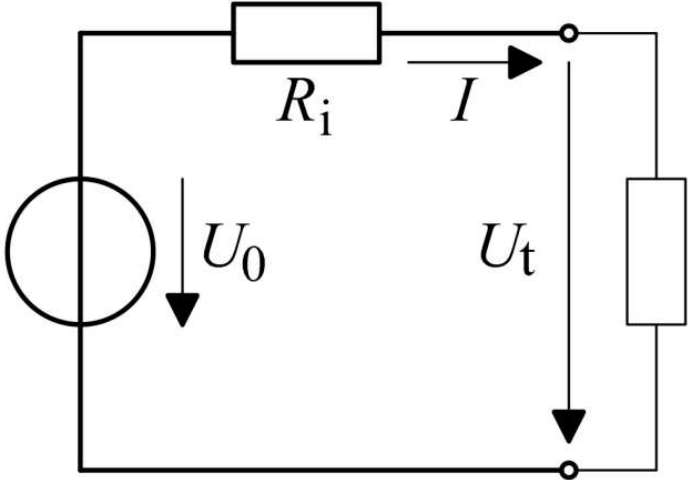


### Voltage source

The following diagram shows the output curves of two voltage sources. The blue curve shows an ideal voltage source. In no-load operation ( $I=0A$ ) it supplies  $U_t=25V$ . At full load ( $I=25A$ ) it still supplies  $U_t=25V$ . The internal resistance  $R_i$  is  $0\Omega$  in this case.

The orange curve shows a real voltage source. In no-load operation ( $I=0A$ ) it supplies also  $U_t=25V$ . At full load ( $I=25A$ ), however, it supplies only  $U_t=20V$ . The internal resistance  $R_i$  in this case is  $\Delta U/\Delta I = 5V/25A = 0.2\Omega$ .

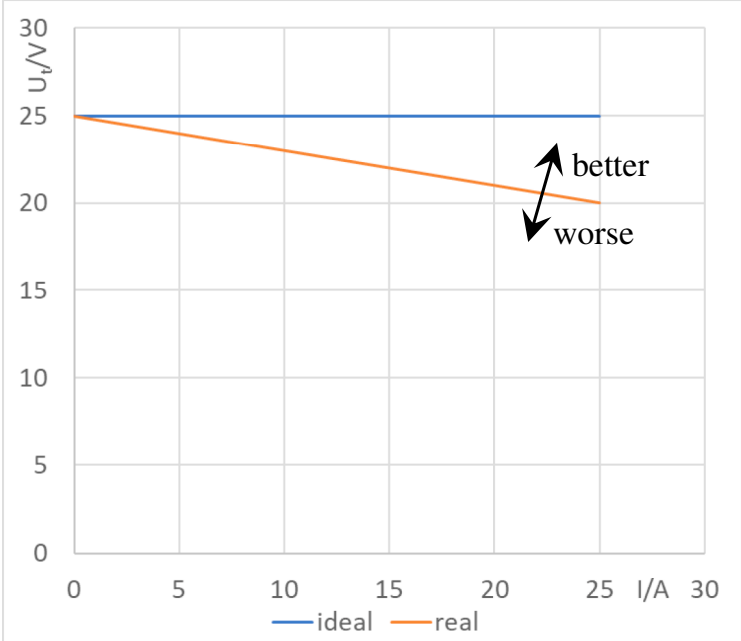You can see that a voltage source is better when its internal resistance  $R_i$  is lower.





**Current source**

The following diagram shows the output curves of two current sources. The blue curve shows an ideal current source. In no-load operation it supplies 25A. For a current source, the short circuit is the no-load condition, that is  $U_t=0V$ . At full load ( $U_t=25V$ ) it still delivers  $I=25A$ . The internal resistance  $R_i$  is infinitely high in this case ( $\infty\Omega$ ), so  $R_i$  is not present.

The orange curve shows a real current source. In no-load operation ( $U_t=0V$ ) it delivers also 25A. At full load ( $U_t=25V$ ), however, it delivers only 20A. The internal resistance  $R_i$  in this case is  $\Delta U/\Delta I = 25V/5A = 5\Omega$ .

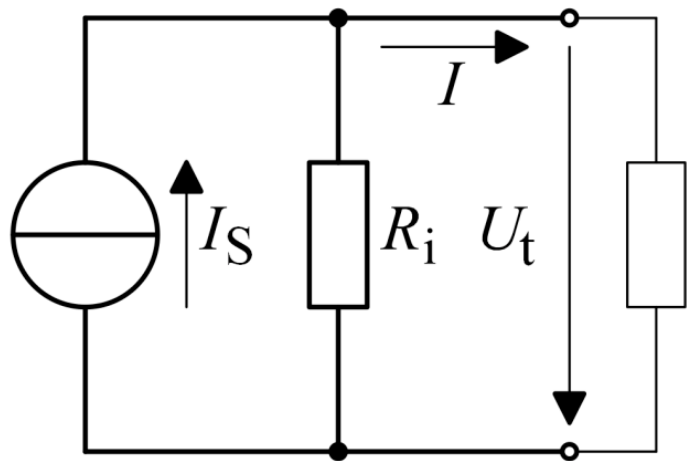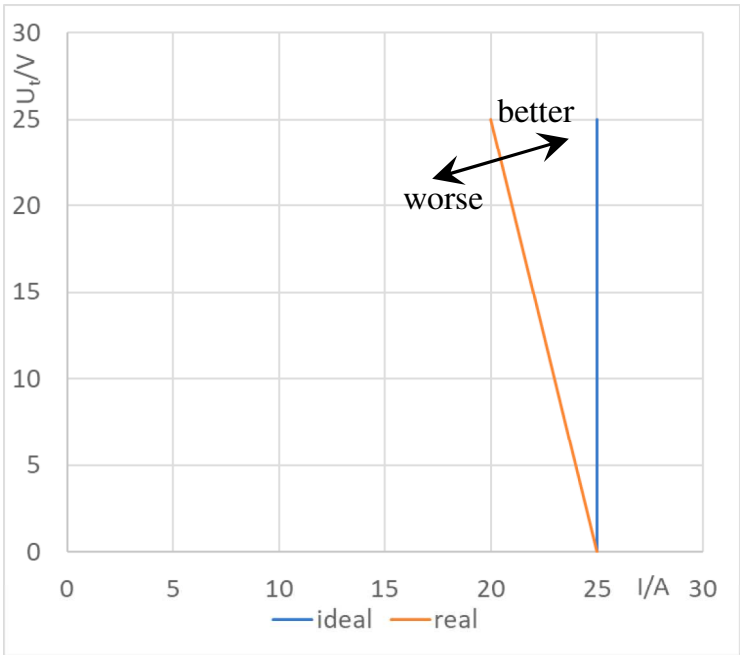You can see that a current source is better if its internal resistance  $R_i$  is higher.





**Real source**

The following diagram shows the curve of a supply. But what is it? Is it a voltage source or a current source?

You can say it is a voltage source.  $U_0$  is 25V. The internal resistance  $R_i$  is  $\Delta U / \Delta I = 25V / 25A = 1\Omega$ .

But you can also say that it is a current source.  $I_S$  is 25A. The internal resistance  $R_i$  is  $\Delta U / \Delta I = 25V / 25A = 1\Omega$ .

And both assumptions are correct! Because you can convert real current sources into real voltage sources, and vice versa. Therefore, you can consider a source to be whatever you like. If the internal resistance is much higher than the load resistance, one would rather speak of a current source. If the internal resistance is much smaller than the load resistance, one would rather speak of a voltage source.

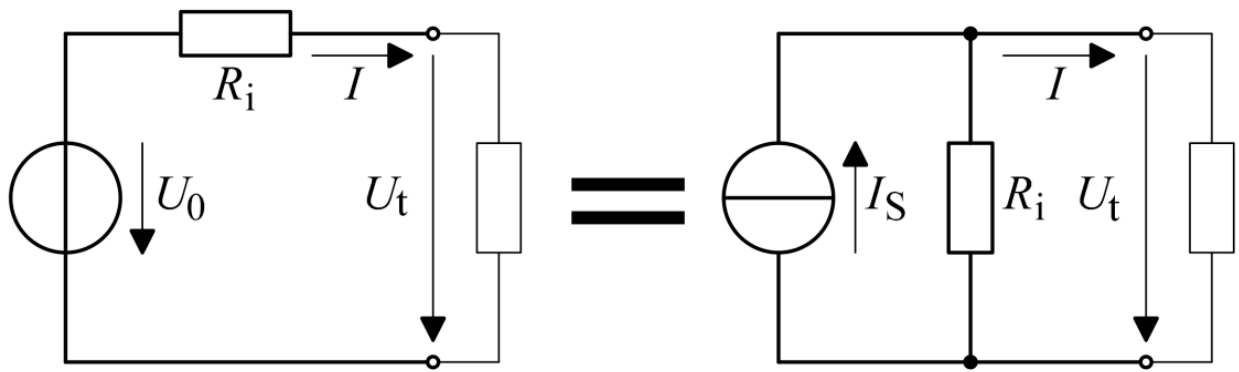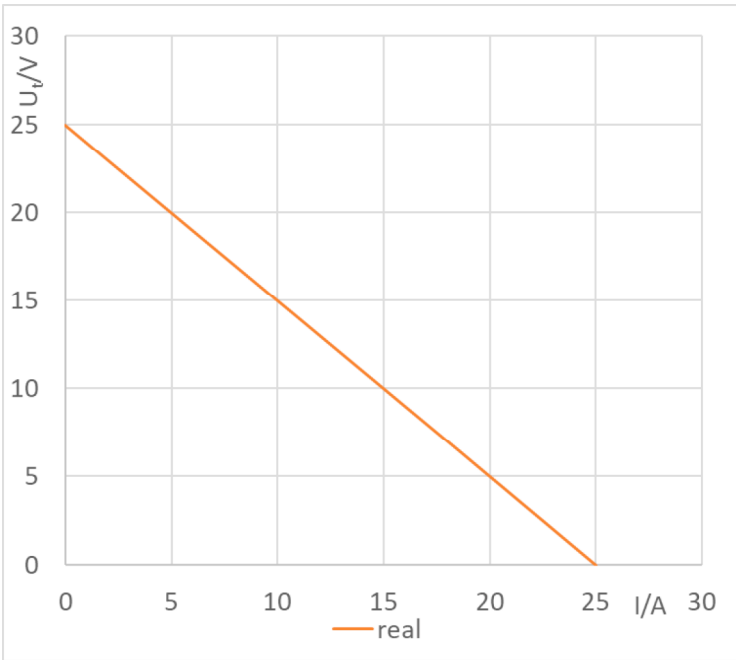

The conversion is done according to the following formulas:


$$U_0 = I_S \cdot R_i \quad \Leftrightarrow \quad I_S = U_0 / R_i$$

## Real current source

The following schematic shows a typical real current source.

At the left, it is connected to an unbalanced mains. This mains voltage is stabilised by a voltage stabiliser, see Technical Newsletter No. 17 for details. Afterwards, the voltage can be manually adjusted by means of an adjustable autotransformer. This voltage is then transformed down to a safe voltage by a LV (Low Voltage) to SELV (Safety Extra Low Voltage) transformer.

Then you see 3 resistors.  $R_{i1}$  symbolises the internal resistance of the source, i.e. the voltage stabilisation and the two transformers.  $100\text{m}\Omega$  is a typical value.  $R_{i2}$  is an additional internal resistance that we will calculate later.  $R_{i3}$  is the resistance of the test setup. It includes not only the device under test but also the wiring. It is typically also around  $100\text{m}\Omega$ .

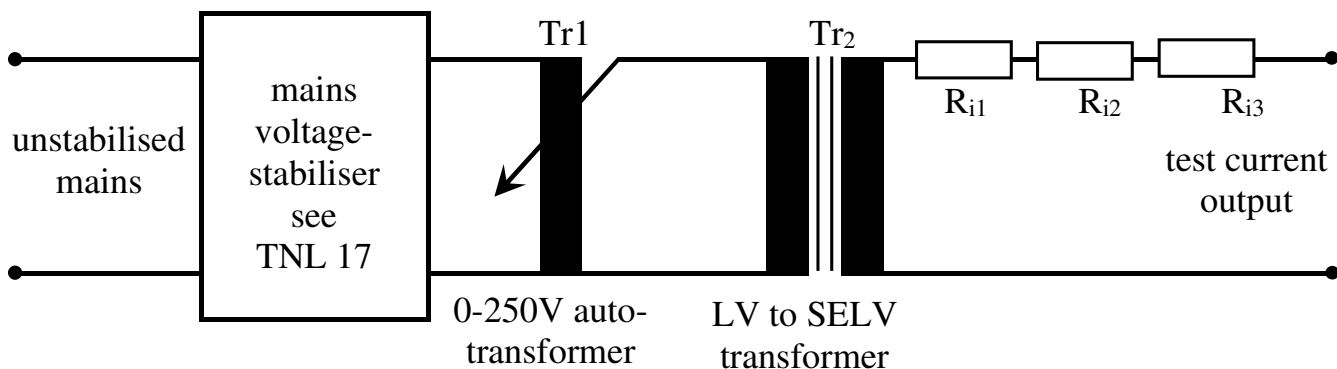

## Is $R_{i2}$ really needed?

Let's do an example calculation. Take  $R_{i1}$  with  $100\text{m}\Omega$ . We leave out  $R_{i2}$ , so it is  $0\Omega$ .  $R_{i3}$  is  $80\text{m}\Omega$  at the beginning of the test (sample is cold). The test current should be  $20\text{A}$ .  $\text{Tr}_1$  must therefore be set so that  $\text{Tr}_2$  supplies  $20\text{A} \cdot (100\text{m}\Omega + 80\text{m}\Omega) = 3.6\text{V}$ .

During the test, the test specimen changes as follows:

- Heating increases the resistance.
- As the temperature rises, the contact pressure decreases (relaxation), which also increases the resistance.

For example, the resistance  $R_{i3}$  increases from  $80\text{m}\Omega$  to  $100\text{m}\Omega$ . But this causes the current to drop from  $20\text{A}$  to  $3.6\text{V} / (100\text{m}\Omega + 100\text{m}\Omega) = 18\text{A}$ !

Now we use  $R_{i2}$  and select  $5\Omega$ . We have to set the voltage at the output of  $\text{Tr}_2$  to  $20\text{A} \cdot (100\text{m}\Omega + 5\Omega + 80\text{m}\Omega) = 103.6\text{V}$  at the beginning of the test. If the resistance of the test object now increases to  $100\text{m}\Omega$ , the current drops from  $20\text{A}$  to  $103.6\text{V} / (100\text{m}\Omega + 5\Omega + 100\text{m}\Omega) = 19.92\text{A}$ . The current is therefore much more constant!